

# AIC Final Project

111511076 陳彥宇

I chose to design a two-stage op amp. The slew rate spec allows us to pick a bias current for the 1<sup>st</sup> stage. Using the equation:

$$\frac{I_{ss}}{C_c} = \text{Slew Rate}$$

Since the slew rate must be larger than 4V/us. I picked a slew rate of 5V/us. Additionally, I placed a 8pF compensation capacitor alongside the 2pF at the output port. Substituting this into the equation and solving it gives:

$$I_{ss} = 50\mu A$$

According to our textbook, *Design of Analog CMOS Integrated Circuit*, the 1<sup>st</sup> stage of the two-stage amplifier should provide high gain and the second stage should provide high output swing. Therefore, the output MOS M8 & M5 should have larger widths. I chose to give M8 11 times the width of M6. This ensures that the amplifier provides a high swing. M1 & M2 must also have large W to provide a large enough gain.

As for the phase margin, the 4.5k compensation resistor is placed to introduce a pole at around 4.42MHz that will drop the gain to unity even faster.

$$\frac{1}{4.5k \times 8p \times 2\pi} = 4.42MHz$$

Sweeping  $V_{in,cm}$  from 0V to 1.8V, reveals that  $V_{in,cm,min} = 0V$ ,  $V_{in,cm,max} = 1.12V$ . However, further testing at  $V_{in,cm} = 1.12V$  reveals that the common-mode gain and gain from VDD will cause CMRR & PSRR to fall below the spec.

After more simulation, 1V turns out to be the maximum input DC voltage. The following are measurement results and simulation waveforms at  $V_{in,cm}$  min, mid, and max.

Supply Voltage (VDD) (V)	1.8		
V <sub>in,cm</sub> (V)	0 (min)	0.2	1.0 (max)
DC Gain (dB)	66.186	68.030	68.759
Unity-gain Frequency (Hz)	158.453M	159.261M	149.552M
Slew Rate (V/us)	7.45	6.27	5.7
Input Common Mode Range(V)	1 - 0 = 1		
Output Max Range (V)	1.15	1.15	1.15
CMRR (dB)	79.471	80.385	67.420
PSRR(VDD) (dB)	89.741	93.763	70.640
Phase Margin ( ° )	65.9604	65.5138	69.8056

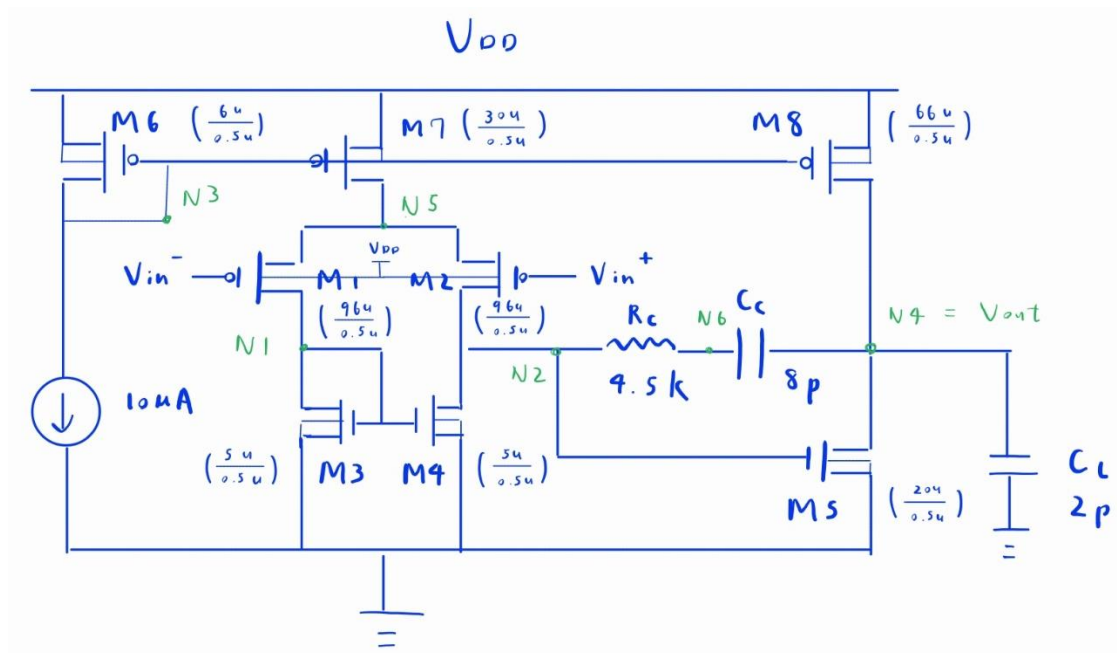


Fig 1. Circuit Schematic

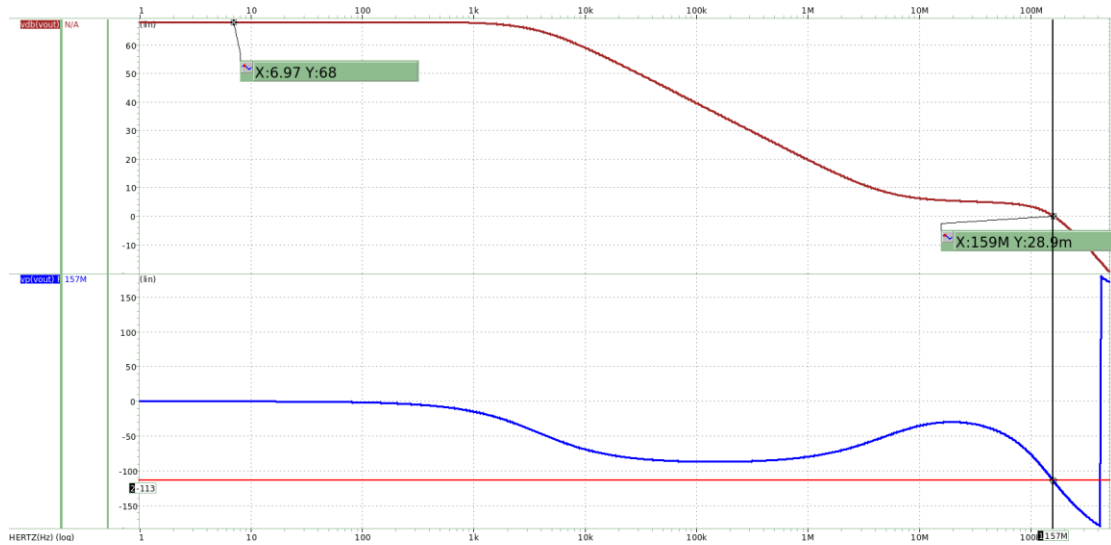


Fig 2. Bode Plot ( $V_{in,cm} = 0.2V$ ) (measures DC gain, PM, Unity-gain Freq.)

```
***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgaindb= 68.0295      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
dcgainv/v= 2.5204k    at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
f3db= 3.7765k
funity= 159.2608x
wgc_phase=-114.4862
pm= 65.5138
*****
```

Fig 3. .ac result ( $V_{in,cm} = 0.2V$ ) (measures DC gain, PM, Unity-gain Freq.)

```
****      small-signal transfer characteristics

| | | | | v(vout)/vsupply      = 51.6769m
| | | | | input resistance at      vsupply = 82.0811k
| | | | | output resistance at v(vout) = 32.3566k
```

Fig 4. Gain from VDD ( $V_{in,cm} = 0.2V$ )

```

****      small-signal transfer characteristics

v(vout)/v_common      = 241.1015m
input resistance at    v_common = 1.000e+20
output resistance at v(vout)      = 32.3566k

```

Fig 5. Common-mode Gain ( $V_{in,cm} = 0.2V$ )



Fig 6. Slew Rate ( $V_{in,cm} = 0.2V$ )

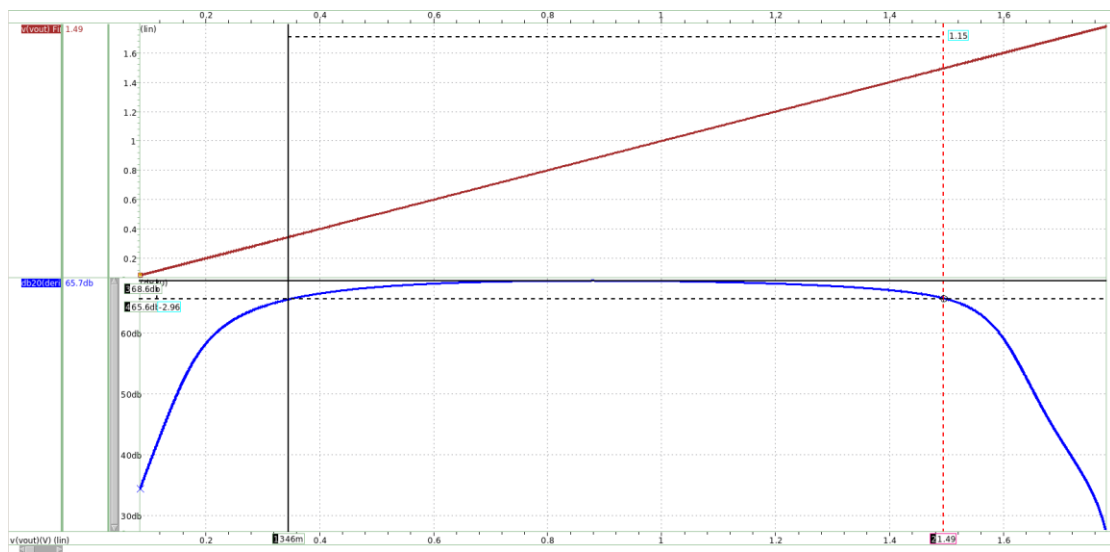


Fig 7. Output Range ( $V_{in,cm} = 0.2V$ )

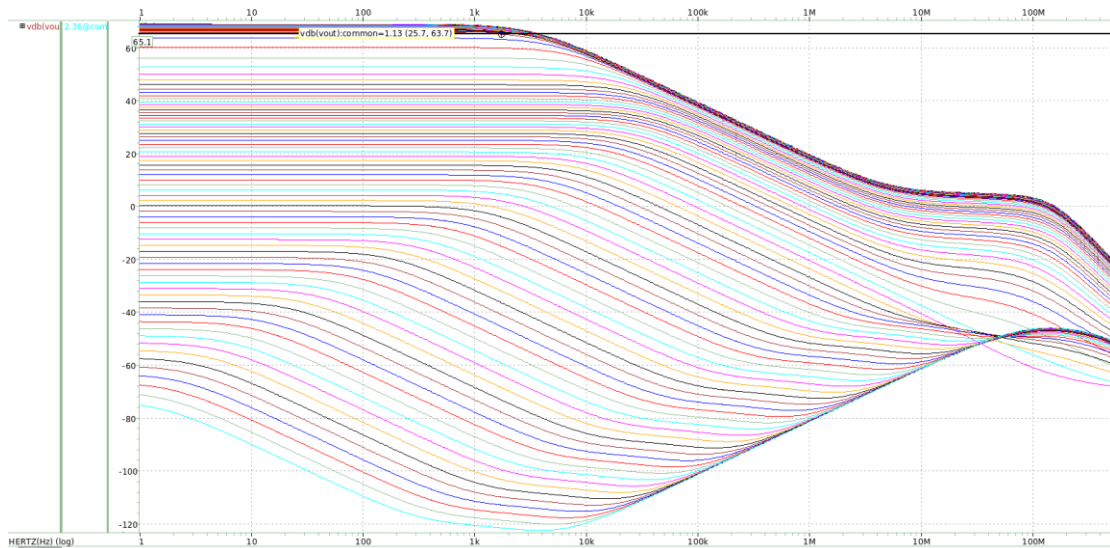


Fig 8. Gain at Different  $V_{in,cm}$

 


Fig 9. Bode Plot ( $\text{Min } V_{in,cm} = 0V$ ) (measures DC gain, PM, Unity-gain Freq.)

```

***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgaindb= 66.1859      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
dcgainv/v= 2.0384k      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
f3db= 4.6520k
funity= 158.4531x
wgc_phase=-114.0396
pm= 65.9604
*****

```

Fig 10. .ac result (Min Vin,cm = 0V) (measures DC gain, PM, Unity-gain Freq.)

```

****      small-signal transfer characteristics
| | | | |
| | | | | v(vout)/vsupply = 66.4105m
| | | | | input resistance at vsupply = 86.8931k
| | | | | output resistance at v(vout) = 32.2265k

```

Fig 11. Gain from VDD (Min Vin,cm = 0V)

```

****      small-signal transfer characteristics
| | | | |
| | | | | v(vout)/v_common = 216.6296m
| | | | | input resistance at v_common = 1.000e+20
| | | | | output resistance at v(vout) = 32.2265k

```

Fig 12. Common-mode Gain (Min Vin,cm = 0V)



Fig 13. Slew Rate (Min  $V_{in,cm} = 0V$ )

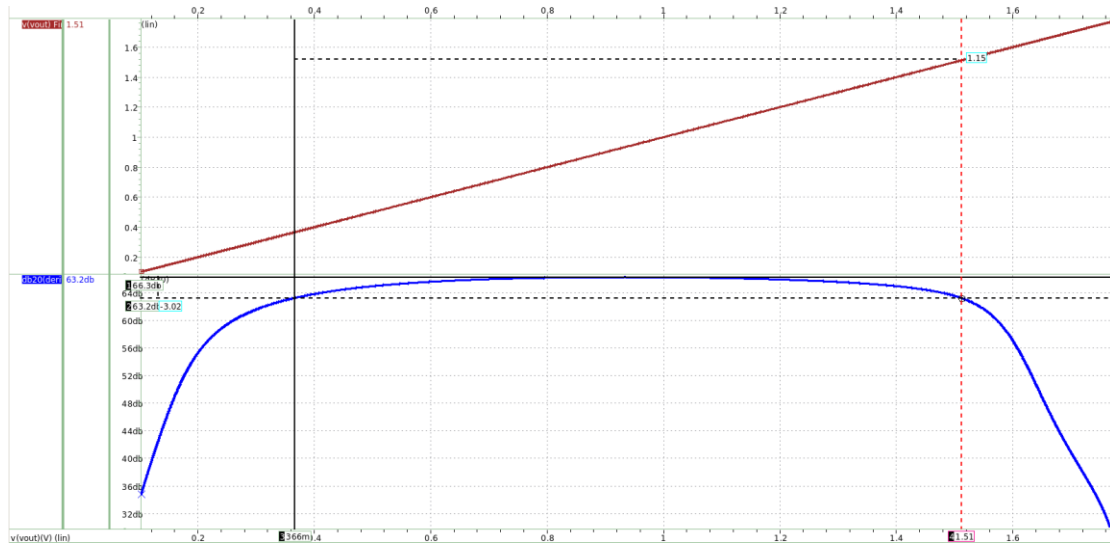


Fig 14. Output Range (Max  $V_{in,cm} = 1V$ )

 


Fig 15. Bode Plot (Min Vin,cm = 0V) (measures DC gain, PM, Unity-gain Freq.)

```

***-----***

***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgaindb= 68.7592      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
dcgainv/v= 2.7413k    at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
f3db= 3.2753k
funity= 149.5517x
wgc_phase=-110.1944
pm= 69.8056
*****

```

Fig 15. .ac result (Max Vin,cm = 1V) (measures DC gain, PM, Unity-gain Freq.)

```

****      small-signal transfer characteristics

| | | | | v(vout)/vsupply = -805.3288m
| | | | | input resistance at vsupply = 26.2472k
| | | | | output resistance at v(vout) = 31.3777k

```

Fig 16. Gain from VDD (Max Vin,cm = 1V)



```

****      small-signal transfer characteristics

v(vout)/v_common      =      1.1667
input resistance at      v_common = 1.000e+20
output resistance at v(vout)      = 31.3777k

```

Fig 17. Common-mode Gain (Max Vin,cm = 1V)

 


Fig 18. Slew Rate (Max Vin,cm = 1V)

 


Fig 19. Output Range (Max Vin,cm = 1V)

# Code:

```
1. ***-----***
2. ***      setting      ***
3. ***-----***
4. .lib "~/U18_HSPICE_Model/mm180_reg18_v124.lib" tt
5. .TEMP 25
6. .op 10u
7. ***-----***
8. ***      simulation      ***
9. ***-----***
10.
11. .option post
12. .option accurate=1
13. .ac DEC 100 1 500Meg
14. .probe AC P(Vout)
15. .probe AC Vdb(Vout)
16. .probe AC VP(Vout)
17. .tran 0.1n 20u
18. .probe tran V(Vout)
19. .tf V(Vout) Vin1
20.
21. ***-----***
22. ***      measure      ***
23. ***-----***
24. .meas AC DCgainDB max Vdb(Vout)
25. .meas AC DCgainV/V max V(Vout)
26. .meas AC f3db when Vdb(Vout)='DCgainDB-3.0'
27. .meas AC funity when Vdb(Vout)='0'
28. .meas AC wgc_phase find VP(Vout) when Vdb(Vout)='0'
29. .meas AC PM param = 'wgc_phase + 180'
30. .meas tran avg_power avg power
31.
32. .meas tran vout_max param = '1.25'
33. .meas tran delta_t trig V(Vout) val='1.25*0.1' rise = 1
34. +targ V(Vout) val='1.25*0.9' rise = 1
35. .meas tran slew_rate param = "(1.25*0.9 - 1.25*0.1) / delta_t"
36.
```

```

37. ***-----***
38. ***      power/input      ***
39. ***-----***
40. Vsupply      VDD      GND      1.8V
41.
42. Vin1      Vin+      GND      DC      1V      AC      0.5V      0
43. Vin2      Vin-      GND      DC      1V      AC      0.5V      180
44.
45. Iss      N3      GND      10u
46. ***-----***
47. ***      circuit      ***
48. ***-----***
49. M1      N1      Vin-      N5      VDD      p_18_mm      w=96u      l=0.5u
50. M2      N2      Vin+      N5      VDD      p_18_mm      w=96u      l=0.5u
51.
52. M3      N1      N1      GND      GND      n_18_mm      w=5u      l=0.5u
53. M4      N2      N1      GND      GND      n_18_mm      w=5u      l=0.5u
54.
55. M5      Vout      N2      GND      GND      n_18_mm      w=20u      l=0.5u
56.
57. M6      N3      N3      VDD      VDD      p_18_mm      w=6u      l=0.5u
58.
59. M7      N5      N3      VDD      VDD      p_18_mm      w=30u      l=0.5u
60.
61. M8      Vout      N3      VDD      VDD      p_18_mm      w=66u      l=0.5u
62.
63. CL      Vout      GND      2p
64. Rc      N2      N6      1
65. Cc      N6      Vout      8p
66.
67. *Original circuit measures DC gain, 3-dB bandwidth, power, unity gain freq., Phase
    Margin
68. .alter
69. *output_swing
70. VDM vid GND offset
71. VCM VCMI GND 0.2V
72. EIN+ Vin+ VCMI vid GND 0.5
73. EIN- Vin- VCMI vid GND -0.5

```

```

74.
75. .alter
76. .alter
77. *measures gain from VDD
78. .tf V(Vout) Vsupply
79. Vsupply VDD GND DC 1.8V AC 1
80.
81. .alter
82. *measures Acn
83. .tf V(Vout) V_common
84. Vin1 Vin+ Common DC 0V
85. Vin2 Vin- Common DC 0V
86. V_common Common GND DC 0.2V AC 0.5
87.
88. .alter
89. *measures Slew Rate, Settling Time
90. .tran 0.1n 20u
91. * PULSE(V1 V2 Tdelay Trise Tfall Pwidth Period)
92. Vin1 Vin+ GND PULSE(0V 1.8V 1us 0ns 0ns 30us 50us)
93. Vin2 Vin- GND DC 0.2V
94.
95. .end
96.
97.

```