

HSPICE Homework #4 of 「類比積體電路導論」

作業繳交截止日期: **Nov.21 , 2024** (上傳 **E3 數位平台** 繳交)

As the amplifier circuits shown in the following Figs. (a), (b), and (c), please perform HSPICE simulations with the device parameters of U18 0.18 μ m CMOS technology. Simulate at TT corner with temperature 25°.

From your simulation results,

- (1) Find the low-frequency voltage gain $A_v = V_{out}/V_{in}$ and the 3-dB bandwidth by using AC analysis for the amplifiers in Figs. (a), (b), and (c), respectively.

	Fig. (a)	Fig. (b)	Fig. (c)
A_v (dB)			
3-dB bandwidth (Hz)			

- (2) Compare both low-frequency voltage gain A_v and 3-dB bandwidth between these two amplifiers in Figs. (a) and (b). Please explain the reasons why they are larger or smaller.
- (3) Compare both output noise voltage and input-referred noise between these two amplifiers in Figs. (a) and (c). Please describe the results you observed and explain whether you think MN2 in Fig. (c) has a **significant impact** on the total output noise. If not, please explain the reason for your assessment.

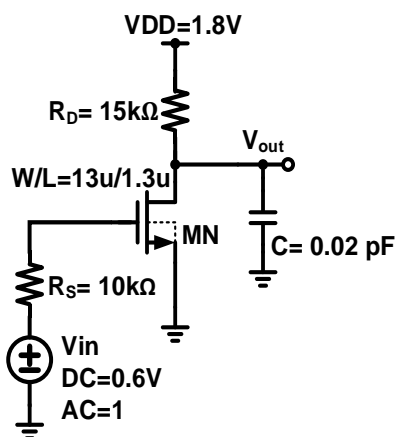


Fig. (a)

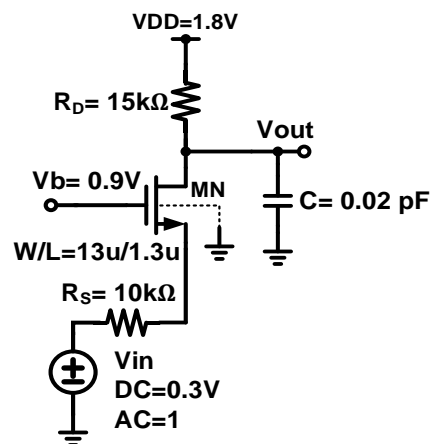


Fig. (b)

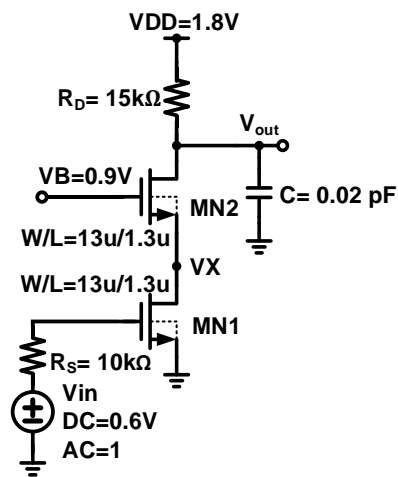


Fig. (c)

HSPICE_HW4：作業需要有以下幾點：

1. HSPICE Code (截圖)
2. Simulation Result (波形繳交背景請用白色，並且波形標示和呈現要清楚)
 - 第 1 題：請展示 $V_{db}(V_{out})$ 的波形並 mark 3db 點
 - 第 3 題：請展示 1~150MHz outnoise & innoise 的波形並將 X 軸(Hz)用 **Log Scale** 呈現。
3. 每個小題的單獨說明
 - 問題(1)** 列成表格
 - 問題(2)** 比較並說明
 - 問題(3)** 比較並說明
 以.pdf 的格式上傳
4. 檔案名稱用「Hspice_HW4_自己的學號」(例如：
Hspice_HW4_0811541)，於作業繳交截止日期前，上傳到指定的 E3 數位平台繳交