

8.1

111511076 陳彥宇

$$20 \log(100) = 40$$

$$(a) \omega_{p2} = 2 \text{ MHz}$$

$$20 \log \frac{2 \text{ M}}{1 \text{ M}} = 20 \cdot 0.301$$

$$= 6.02$$

$$40 - 6.02 = 33.98$$

$$33.98 - 40 \log \frac{x \text{ M}}{2 \text{ M}} = 0$$

$$x = 14.1426$$

$$14.143 \text{ MHz} \#$$

$$(b) \omega_{p2} = 3 \text{ MHz}$$

$$20 \log \frac{3 \text{ M}}{1 \text{ M}} = 9.5424$$

$$40 - 9.5424 = 30.4576$$

$$30.4576 - 40 \log \frac{x \text{ M}}{3 \text{ M}} = 0$$

$$x = 17.3205$$

$$\text{Unity-gain freq.} = 17.3205 \text{ MHz}$$

$$\text{Phase reaches } -180^\circ \text{ at } 10 \cdot \omega_{p2} = 30 \text{ MHz}$$

$$-\arctan\left(\frac{17.3205 \text{ M}}{1 \text{ M}}\right) - \arctan\left(\frac{17.3205 \text{ M}}{3 \text{ M}}\right) = -166.8692^\circ$$

$$-166.8692^\circ + 180^\circ = 13.1308$$

$$= 13.131^\circ \#$$

8.2

$$(a) r_{o2} = \frac{1}{0.1 \cdot 0.25 \text{ m}} = 40 \text{ k}$$

$$r_{o3} = \frac{1}{0.2 \cdot 0.25 \text{ m}} = 20 \text{ k}$$

$$R_x = (r_{o1} + r_{o2}) \parallel r_{o3}$$

$$= 16 \text{ k}$$

$$\frac{1}{\omega_{pX}} = R_x C_x = 13.3333 \text{ n}$$

$$\omega_{pX} = 62.5 \text{ M rad/s} \#$$

$$g_{m4} = \sqrt{2 \cdot 0.13428 \text{ m} \cdot 100 \cdot 0.5 \text{ m}} = 3.6644 \text{ m}$$

$$R_Y = \frac{1}{g_{m4}} \parallel r_{o4} = 269.221 \Omega$$

$$\frac{1}{\omega_{pY}} = R_Y C_Y = 269.221 \text{ p}$$

$$\omega_{pY} = 3.7144 \text{ G rad/s} \#$$

$$g_{m2} = \sqrt{2 \cdot 0.13428 \text{ m} \cdot 100 \cdot 0.25 \text{ m}} = 2.59114 \text{ m}$$

$$\begin{aligned} (b) \text{ DC gain} &= \frac{g_{m2}}{2} (2r_{o2} \parallel r_{o3}) \frac{r_{o4}}{\frac{1}{g_{m4}} + r_{o4}} \\ &= 20.444 \\ &= 26.2113 \text{ dB} \end{aligned}$$



$$26.2113 \text{ dB} - 20 \log \left(\frac{\chi}{62.5 \text{ M}} \right) = 0$$

$$\chi = 1.2117 \text{ G rad/s}$$

$$-\arctan \left(\frac{1.2117 \text{ G}}{62.5 \text{ M}} \right) - \arctan \left(\frac{1.2117 \text{ G}}{3.7144 \text{ G}} \right) = -106.182^\circ$$

$$-106.182 + 180 = 73.818^\circ \quad \#$$

(c) $| \beta A | \text{ (dB)}$

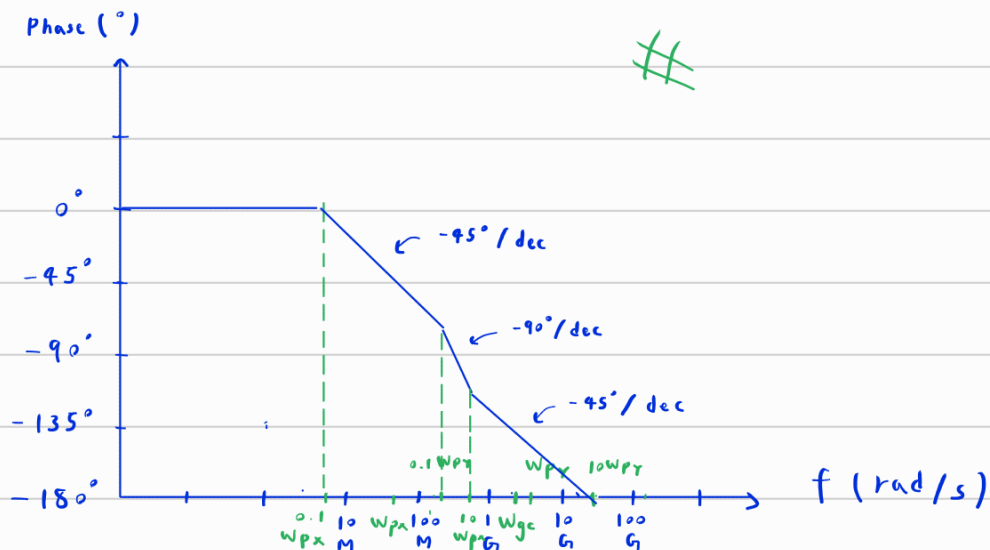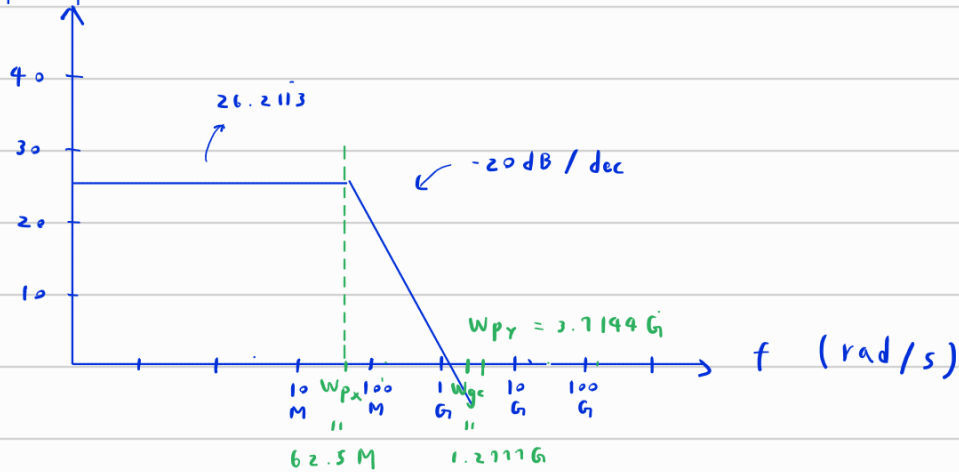

$$(d) \quad x + 180^\circ = 60^\circ$$

$$x = -120^\circ$$

$$-\arctan\left(\frac{1.2777 G}{62.5 M}\right) - \arctan\left(\frac{1.2777 G}{\omega_{pY'}}\right) = -120^\circ$$


$$\omega_{pY'} = 1.98257 \text{ rad/s}$$

$$\frac{1}{\omega_{pY'}} = 504.3963 \text{ p}$$

$$237.9590 \text{ p} \div R_Y = 1.874 \text{ pF} \quad \#$$

8.3

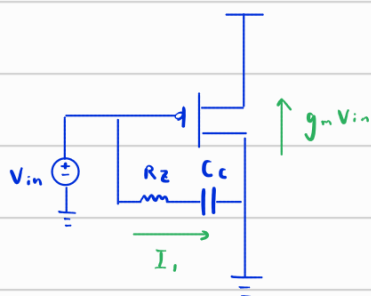(a) To determine the zero, ground V_{out}



$$I_1 = \frac{V_{in}}{R_Z + \frac{1}{sC_C}} = g_m V_{in}$$

$$\frac{1}{R_Z + \frac{1}{sC_C}} = g_m$$

$$1 = g_m R_Z + g_m \frac{1}{sC_C}$$

$$sC_C = g_m R_Z sC_C + g_m$$

$$s(C_C - g_m R_Z C_C) = g_m$$

$$sC_C(1 - g_m R_Z) = g_m$$

$$s = \frac{g_m}{C_C(1 - g_m R_Z)}$$

$$\omega_Z = \frac{1}{C_C \left(\frac{1}{g_m} - R_Z \right)} \quad \#$$

(b) This leads to a positive zero in the right half plane. The zero contributes negative phase shift, moving ω_{pc} closer to the origin. The zero also slows down the drop of the magnitude, moving ω_{gc} further away from the origin. Both changes are undesirable because we want $\omega_{gc} < \omega_{pc}$ #

to keep the circuit stable.

(c) If $\frac{1}{C_c \left(\frac{1}{g_{m1}} - R_z \right)} = \frac{-g_{m1}}{C_L}$, then the pole and zero cancel out

$$-g_{m1} C_c \left(\frac{1}{g_{m1}} - R_z \right) = C_L$$

$$C_c (-1 + g_{m1} R_z) = C_L$$

$$-C_c + C_c g_{m1} R_z = C_L$$

$$R_z = \frac{C_L + C_c}{g_{m1} C_c} \quad \#$$