

$$V_{\text{out}} = \frac{g_{n_2} - g_{n_1}}{\frac{1}{r_{01}} + g_{n_2} + \frac{1}{r_{02}}} V_{\text{in}}$$

$$V_{gsz} = V_{out} - i_{x} R_{D}$$

$$V_{gsz} = V_{out} - \left(-g_{n} V_{gsz} - \frac{V_{out}}{r_{oz}}\right) R_{D}$$

$$V_{gsz} = V_{out} + g_{nz} V_{gsz} R_{D} + \frac{V_{out}}{r_{oz}} R_{D}$$

$$\left(1 - g_{nz} R_{D}\right) V_{gsz} = \left(1 + \frac{R_{D}}{r_{oz}}\right) V_{out}$$


$$V_{gsz} = \frac{r_{oz} + R_{D}}{r_{oz} - g_{nz} r_{oz} R_{D}} V_{out}$$

$$g_{m_1} V_{gs_1} + \frac{V_X}{r_{o_1}} = -g_{m_2} V_{gs_2} - \frac{V_{out}}{r_{o_2}}$$

$$g_{m_1} V_{in} + \frac{V_{gs_2}}{r_{o_1}} = -g_{m_2} V_{gs_2} - \frac{V_{out}}{r_{o_2}}$$

$$g_{n_1}V_{in} + \frac{1}{r_{o_1}} \frac{r_{o_2} + R_D}{r_{o_2} - g_{n_2} r_{o_2} R_D} V_{out} = -g_{n_2} \frac{r_{o_2} + R_D}{r_{o_2} - g_{n_2} r_{o_2} R_D} V_{out} - \frac{V_{out}}{r_{o_2}}$$
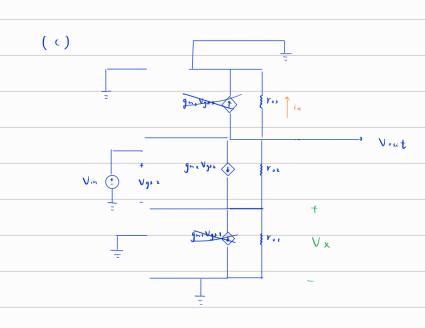
$$g_{n_1}V_{in} = \left(-\frac{r_{o_2} + R_D}{r_{o_1} r_{o_2} - g_{n_2} r_{o_1} R_D} - \frac{g_{n_2} r_{o_2} + g_{n_2} R_D}{r_{o_2} - g_{n_2} r_{o_2} R_D} - \frac{1}{r_{o_2}}\right) V_{out}$$



$$g_{m3}Vg_{s3} + ix + g_{m2}Vg_{s2} + \frac{V_{04}t - Vx}{Y_{02}} = 0$$

$$g_{m2}Vg_{s2} + \frac{V_{04}t - Vx}{Y_{02}} = \frac{Vx}{Y_{01}}$$

$$\frac{Vx}{Y_{01}} = -ix \qquad Vx = -Y_{01}ix$$

$$Vg_{s2} = V_{in} - Vx$$

$$= V_{01} - V_{04}t + \frac{Y_{01}}{Y_{01}tY_{02}}$$

$$Vg_{s3} = 0V$$

Vgs, = 0V

$$-g_{n3} \times g_{33} + \frac{o - V_{out}}{V_{o3}} = g_{n2} \times g_{32} + \frac{V_{out} - V_{A}}{V_{o2}}$$

$$g_{n2} \times g_{32} + \frac{V_{out} - V_{A}}{V_{o2}} = g_{n1} \times g_{32} + \frac{V_{x}}{V_{o1}}$$

$$V_{X} = -\frac{r_{01}}{r_{03}} \quad V_{0N} + \frac{V_{0N} + V_{X}}{r_{02}}$$

$$-g_{m2}V_{in} = \frac{V_{0N} + \frac{V_{0N} + V_{X}}{r_{03}} - g_{m2}\left(-\frac{V_{01}}{r_{03}}V_{0N}t\right) + \frac{V_{0N} + \frac{V_{0N}}{r_{02}} - \frac{1}{r_{03}}\left(-\frac{r_{01}}{r_{03}}V_{0N}t\right)$$

$$-g_{m2}V_{in} = \left(-\frac{1}{r_{03}} + \frac{1}{r_{03}} + g_{m2}\frac{r_{03}}{r_{03}} + \frac{r_{03}}{r_{04}r_{03}}\right) V_{0N} + \frac{V_{0N} + \frac{V_{0N}}{r_{03}}}{V_{0N}} = \frac{g_{m2}r_{02}r_{03}}{r_{02} + g_{m2}r_{02}r_{03} + r_{03} + r_{03}}$$

V <sub>DD</sub> = 3 V
Cox = 3.9 to = 3.83613 × 10-1 F/cm2
Дn = 350 cm*/V/s Vtn= 0.7
Mp = 100 cm = 1 V/s Vtp = -0.8
K' = 0.13428 mA / V" K'p = 0.03837 mA/ V"
K1,2 = 20.142 nA /V" \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \
Ka, 4 = 1.279 HA/V2 Ap = 0.2
ks = 10.071 mA/V*

(0)

$$A_{V} = -3.11348 \text{ m} \cdot (r_{01} || r_{03} || \frac{1}{9^{-3.4}})$$

$$= -3.62812 \text{ V/V}$$

$$= -3.628 \text{ V/V} \#$$

( c ) 0.25 m = 1 + 1.279 m + Vovs Vovs = 0.62524 V (i) Vos 1.42524V Vb=1.57476 V Vd3 mx = 1.57476+0.8 Vinna = 3.07976V (con't be larger than Voo) Vin, cm max = min { Voo - Vov3 + Vth, , VDO } = 3 Vinjem min = Vess min + Ngs, = 0.315 + 0.8576 = 1.1126 1.173 V & Vin, cm & 3 V # (ii) Vout, max = Vd3 max = 2,31476 Vout min = 1.2 -0.7 = 0.3 2 (2,3747 6 -0.5) = 3,7495 2 = 3.750 V # (iii)  $\gamma_{03} = \frac{1}{\lambda_0 I_0} = \frac{1}{0.1 \cdot 0.25 m} = 40 \text{ k}$ rol = 1 = 1 = 1 = 20k 9m, = = J2 - 20. 142 m - 0.25m = 3.11348 m Av = - 3.17348 m (40k || 20k) = -42,313 V/V # 2.3 K'p = 0.03837 HA/ VE K' = 0.13428 mA / V" IDS = ID6 = 0.4 mA (~) Kn = 16.1136 mA/V2 Kp = 4.6094 mA/V2 ID3 = 109 = 0.1 m A 9m1 = Jzkn+0.5m = 4.01419 m 9m3 = J2 kp + 0.1 m = 0.95962 m = 1.04208 k Vos = 1 1 2.5 k r.3 = 1 = 50k You = 1 20 K

Av = - gmi . ( - 1 | 1 | ro, | | ros)

= -3.618 V/V #

= -3.6176

(b)
$$I_{DS} = 0.4 \text{ mA} = \frac{1}{2} \cdot 4.6044 \text{ m} \cdot \text{Vovs}^{2}$$

$$V_{ovs} = 0.41683$$

$$V_{sqs} = 1.21683$$

$$3 - 1.21683 = 1.78317$$

$$V_{b} = 1.783 \text{ #}$$
(c)
$$V_{out}|_{1,2} \text{ max} = \min \left\{ V_{b} + |V_{thsp}| , V_{po} - |V_{thsp}| \right\}$$

Vout 
$$I_{1,2}$$
 max = min {  $V_{0} + |V_{0}|_{1}$  ,  $V_{00} - |V_{0}|_{1}$  }

= min {  $I \cdot 183 + 0.8$  ,  $3 - 0.8$  }

= 2 \cdot 2

0 \cdot 6 \cdot A =  $\frac{1}{2}$  \cdot |6 \cdot |136 m \cdot (V\_{3}) - 0.7 ) 2

V\_{3} \cdot |  $I_{0} = 0.1 \text{ mA} = 0.97287$ 

0 \cdot 2 mA =  $\frac{1}{2}$  \cdot 9 \cdot 6 094 m \cdot (V\_{3}) = 0.8 ) 2

V\_{3} \sqrt{  $I_{0} = 0.1 \text{ mA} = 1.09474}$  (No current goes through Mq)

V\_{0} \text{  $I_{1,2} = min = max {  $V_{12} = min + V_{3} = 1.09474}$  (No current goes through Mq)

= max {  $0.9 + 0.97289 - 0.7$  ,  $3 - 1.09474$  }

= max {  $0.9 + 0.97289 - 0.7$  ,  $3 - 1.09474$  }

=  $1.90829$$ 

2 (2.2-1.90529) = 0.38942