

Homework #1 of 「類比積體電路導論」

作業繳交截止日期: Oct. 3, 2024 12:00 (上傳 E3 數位平台 繳交)

本次作業共三大題, 1.1~1.3

請將作業轉成一個 PDF 檔案(file size 小於 10MB), 檔名請使用

「AIC_HW1_自己的學號」(例如: AIC_HW1_109700018), 於作業繳

交截止日期/時間前, 上傳到指定的 E3 數位平台 繳交。

Unless otherwise stated, in the following problems, use the device data shown in Table 1 and assume that $V_{DD} = 3V$. The Dielectric constant of gate oxide is 3.9 and $\epsilon_o = 8.854 \times 10^{-12} F/m$.

Table 1. Level 1 SPICE models for NMOS and PMOS devices.

NMOS Model			
LEVEL = 1	VTO = 0.7	GAMMA = 0.45	PHI = 0.9
NSUB = 9e+14	LD = 0.08e-6	UO = 350	LAMBDA = 0.1
TOX = 9e-9	PB = 0.9	CJ = 0.56e-3	CJSW = 0.35e-11
MJ = 0.45	MJSW = 0.2	CGDO = 0.4e-9	JS = 1.0e-8
PMOS Model			
LEVEL = 1	VTO = -0.8	GAMMA = 0.4	PHI = 0.8
NSUB = 5e+14	LD = 0.09e-6	UO = 100	LAMBDA = 0.2
TOX = 9e-9	PB = 0.9	CJ = 0.94e-3	CJSW = 0.32e-11
MJ = 0.5	MJSW = 0.3	CGDO = 0.3e-9	JS = 0.5e-8

VTO: threshold voltage with zero V_{SB} (unit: V)

GAMMA: body-effect coefficient (unit: $V^{1/2}$)

PHI: $2\Phi_F$ (unit: V)

TOX: gate-oxide thickness (unit: m)

NSUB: substrate doping (unit: cm^{-3})

LD: source/drain side diffusion (unit: m)

UO: channel mobility (unit: $cm^2/V/s$)

LAMBDA: channel-length modulation coefficient (unit: V^{-1})

CJ: source/drain bottom-plate junction capacitance per unit area (unit: F/m^2)

CJSW: source/drain sidewall junction capacitance per unit length (unit: F/m)

PB: source/drain junction built-in potential (unit: V)

MJ: exponent in CJ equation (unitless)

MJSW: exponent in CJSW equation (unitless)

CGDO: gate-drain overlap capacitance per unit width (unit: F/m)

CGSO: gate-source overlap capacitance per unit width (unit: F/m)

JS: source/drain leakage current per unit area (unit: A/m^2)

- 1.1 Assuming all MOSFETs are in saturation with $\lambda \neq 0$ and $\gamma = 0$, calculate the small-signal voltage gain of each circuit in Fig. 1. 本題限定使用 R_x , g_{m_x} , r_{o_x} 電晶體參數符號進行推導 (40 pts)

 


Figure 1.

- 1.2 A source follower can operate as a level shifter. Suppose the circuit of Fig. 2 is designed to shift the voltage level by 1 V, i.e., $V_{in} - V_{out} = 1V$. The body of M_1 and M_2 is connected to GND. (30 pts)
- Calculate the dimensions of M_1 and M_2 if $I_{D1} = I_{D2} = 0.5$ mA, $V_{GS2} - V_{GS1} = 0.5$ V, and $\lambda = \gamma = 0$.
 - Repeat part (a) if $\lambda = 0$, $\gamma = 0.45$ V⁻¹ and $V_{in} = 2.5$ V.
 - If $I_{D1} = I_{D2} = 0.5$ mA, $V_{GS2} - V_{GS1} = 0.5$ V and $\lambda = 0$, $\gamma = 0.45$ V⁻¹, what is the minimum input voltage for which M_2 remains saturated? Assume dimensions of M_1 and M_2 remain part(b).

 


Figure 2

1.3 Suppose the common-source stage of Fig. 3 is to provide an output swing from 1 V to 2 V. Assume that $W/L = 60/0.5$, $R_D = 2 \text{ k}\Omega$. Also, use $\lambda = \gamma = 0$ for bias purpose and $\lambda \neq 0, \gamma = 0$ for small signal analysis. (30 pts)

- (a) Calculate the input voltages that yield $V_{\text{out}} = 1 \text{ V}$ and $V_{\text{out}} = 2 \text{ V}$.
- (b) Calculate the drain current and the transconductance of M_1 for both cases.
- (c) How much does the small-signal gain for the output voltage equal 1 V and 2 V? (Variation of small-signal gain can be viewed as nonlinearity.)

 


Figure 3