

Homework #7 of 「類比積體電路導論」

作業繳交截止日期: **Dec. 5, 2024 12:00** (上傳E3數位平台繳交)

本次作業共兩大題，7.1~7.2

請將作業轉成一個PDF檔案(file size小於10MB)，檔名請使用

「AIC_HW7_自己的學號」(例如: AIC_HW7_109700018)，於作業繳

交截止日期/時間前，上傳到指定的E3數位平台繳交。

Unless otherwise stated, in the following problems, use the device data shown in Table 1 and assume that $V_{DD}=3V$. The Dielectric constant of gate oxide is 3.9 and $\epsilon_0=8.854\times 10^{-12}F/m$.

Table 1. Level 1 SPICE models for NMOS and PMOS devices.

NMOS Model			
LEVEL = 1	VTO = 0.7	GAMMA = 0.45	PHI = 0.9
NSUB = 9e+14	LD = 0.08e-6	UO = 350	LAMBDA = 0.1
TOX = 9e-9	PB = 0.9	CJ = 0.56e-3	CJSW = 0.35e-11
MJ = 0.45	MJSW = 0.2	CGDO = 0.4e-9	JS = 1.0e-8
PMOS Model			
LEVEL = 1	VTO = -0.8	GAMMA = 0.4	PHI = 0.8
NSUB = 5e+14	LD = 0.09e-6	UO = 100	LAMBDA = 0.2
TOX = 9e-9	PB = 0.9	CJ = 0.94e-3	CJSW = 0.32e-11
MJ = 0.5	MJSW = 0.3	CGDO = 0.3e-9	JS = 0.5e-8

VTO: threshold voltage with zero V_{SB} (unit: V)

GAMMA: body-effect coefficient (unit: $V^{1/2}$)

PHI: $2\Phi_F$ (unit: V)

TOX: gate-oxide thickness (unit: m)

NSUB: substrate doping (unit: cm^{-3})

LD: source/drain side diffusion (unit: m)

UO: channel mobility (unit: $cm^2/V/s$)

LAMBDA: channel-length modulation coefficient (unit: V^{-1})

CJ: source/drain bottom-plate junction capacitance per unit area (unit: F/m²)

CJSW: source/drain sidewall junction capacitance per unit length (unit: F/m)

PB: source/drain junction built-in potential (unit: V)

MJ: exponent in CJ equation (unitless)

MJSW: exponent in CJSW equation (unitless)

CGDO: gate-drain overlap capacitance per unit width (unit: F/m)

CGSO: gate-source overlap capacitance per unit width (unit: F/m)

JS: source/drain leakage current per unit area (unit: A/m²)

7.1 In this problem, we design a two-stage op amp based on topology shown in Fig 7.1. Assume a power budget of 6mW, a required output swing of 2.4V, and $L_{\text{eff}} = 0.5\mu\text{m}$ for all devices. Assume $\lambda=\gamma=0$ for bias purpose and $\gamma=0, \lambda\neq 0$ for small signal analysis.

- (a) Allocating a current of 1 mA to the output stage and roughly equal overdrive voltages to M_5 and M_6 , determine $(W/L)_5$ and $(W/L)_6$.

Note that the gate-source capacitance of M_5 is in the signal path, whereas that of M_6 is not. Thus, M_6 can be quite a lot larger than M_5 .

- (b) Calculate the small-signal gain of the output stage. (calculate the 2nd stage gain only).

- (c) With the remaining 1 mA flowing through M_7 , determine the aspect ratio of M_3 (and M_4) such that $V_{GS3} = V_{GS5}$.

This is to guarantee that if $V_{\text{in}} = 0$ and hence $V_X = V_Y$, then M_5 carries the expected current.

- (d) Calculate the aspect ratios of M_1 and M_2 such that the overall voltage gain of the op amp is equal to 400.

 


Fig.7.1

7.2 In the op amp of Fig. 7.2, $(W/L)_{1-8} = 120 \mu\text{m}/0.5 \mu\text{m}$, $I_{SS} = 1 \text{ mA}$, and $V_{b1} = 1.7 \text{ V}$. Assume that $\lambda = \gamma = 0$.

- What is the maximum allowable input CM level?
- What is V_X ?
- What is the maximum allowable output swing if the gate of M_2 is connected to the output?
- What is the acceptable range of V_{b2} ?

 


Fig.7.2