

## Homework #8 of 「類比積體電路導論」

作業繳交截止日期: **Dec. 12, 2024 12:00** (上傳E3數位平台繳交)

本次作業共兩大題, 8.1~8.3

請將作業轉成一個 PDF 檔案(file size 小於 10MB), 檔名請使用

「AIC\_HW8\_自己的學號」(例如: AIC\_HW8\_109700018), 於作業繳

交截止日期/時間前, 上傳到指定的E3 數位平台繳交。

Unless otherwise stated, in the following problems, use the device data shown in Table 1 and assume that  $V_{DD}=3V$ . The Dielectric constant of gate oxide is 3.9 and  $\epsilon_0=8.854 \times 10^{-12} F/m$ .

Table 1. Level 1 SPICE models for NMOS and PMOS devices.

|              |              |               |                 |
|--------------|--------------|---------------|-----------------|
| NMOS Model   |              |               |                 |
| LEVEL = 1    | VTO = 0.7    | GAMMA = 0.45  | PHI = 0.9       |
| NSUB = 9e+14 | LD = 0.08e-6 | UO = 350      | LAMBDA = 0.1    |
| TOX = 9e-9   | PB = 0.9     | CJ = 0.56e-3  | CJSW = 0.35e-11 |
| MJ = 0.45    | MJSW = 0.2   | CGDO = 0.4e-9 | JS = 1.0e-8     |
| PMOS Model   |              |               |                 |
| LEVEL = 1    | VTO = -0.8   | GAMMA = 0.4   | PHI = 0.8       |
| NSUB = 5e+14 | LD = 0.09e-6 | UO = 100      | LAMBDA = 0.2    |
| TOX = 9e-9   | PB = 0.9     | CJ = 0.94e-3  | CJSW = 0.32e-11 |
| MJ = 0.5     | MJSW = 0.3   | CGDO = 0.3e-9 | JS = 0.5e-8     |

VTO: threshold voltage with zero  $V_{SB}$  (unit: V)

GAMMA: body-effect coefficient (unit:  $V^{1/2}$ )

PHI:  $2\Phi_F$  (unit: V)

TOX: gate-oxide thickness (unit: m)

NSUB: substrate doping (unit:  $cm^{-3}$ )

LD: source/drain side diffusion (unit: m)

UO: channel mobility (unit:  $cm^2/V/s$ )

LAMBDA: channel-length modulation coefficient (unit:  $V^{-1}$ )

CJ: source/drain bottom-plate junction capacitance per unit area (unit: F/m<sup>2</sup>)

CJSW: source/drain sidewall junction capacitance per unit length (unit: F/m)

PB: source/drain junction built-in potential (unit: V)

MJ: exponent in CJ equation (unitless)

MJSW: exponent in CJSW equation (unitless)

CGDO: gate-drain overlap capacitance per unit width (unit: F/m)

CGSO: gate-source overlap capacitance per unit width (unit: F/m)


JS: source/drain leakage current per unit area (unit: A/m<sup>2</sup>)

**8.1 A feedback amplifier has a loop gain of 100 and two poles at  $\omega_{p1}$  and  $\omega_{p2}$ . For  $\omega_{p1}=1$  MHz. (Hint: can use Bode plot)**

- (a) Calculate the unit gain frequency if  $\omega_{p2} = 2\omega_{p1}$ .
- (b) Calculate the phase margin if  $\omega_{p2} = 3\omega_{p1}$ .

**8.2 Consider the amplifier of Fig. 1, where  $(W/L)_{1-4} = 50/0.5$  and  $I_{SS} = I_1 = 0.5$  mA. Assume that  $C_X = C_Y = 1$  pF and all the transistor capacitances can be neglected.**

- (a) Estimate the poles at nodes X and Y by multiplying the small-signal resistance and capacitance to ground.
- (b) What is the phase margin for unity-gain feedback?
- (c) Depict the Bode plot. Specify the low-frequency gain, the frequency of pole X, the frequency of Pole Y and the unit-gain frequency.
- (d) What is the maximum tolerable value of  $C_Y$  that yields a phase margin of  $60^\circ$  for unity-gain feedback?

 

**Fig. 1**

8.3 For the circuit shown in Fig.2.

 


Fig. 2

- (a) Find the zero of the circuit and express it in terms of a function.
- (b) How will this zero affect the phase margin if  $R_z=0$ ? Explain it.
- (c) What value can we choose for  $R_z$  to eliminate the zero?