
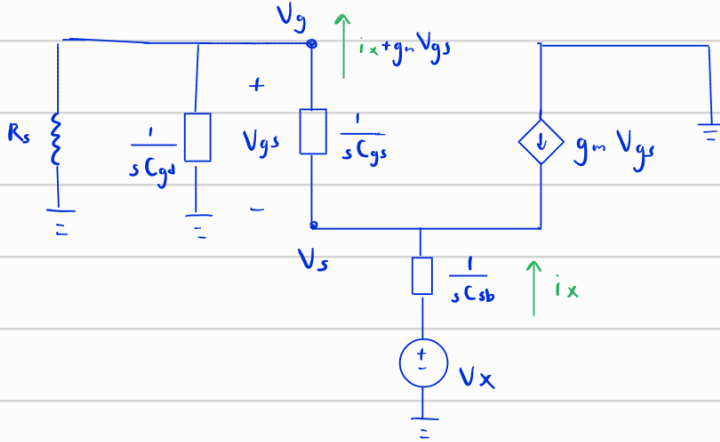


4.1

(a)

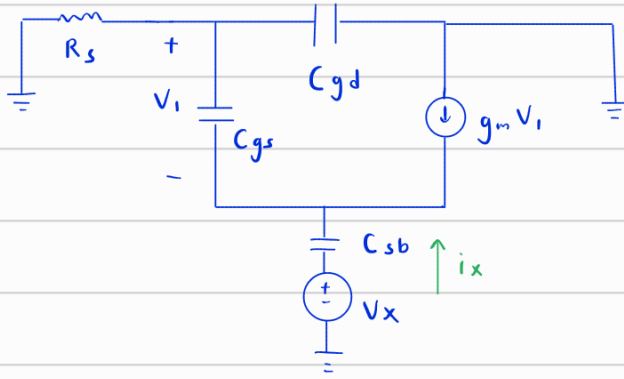

$$C_{ov} = C_{ox} L_0$$

$$C_{gd} = C_{gd0} W$$

$$C_{gs} = \frac{2}{3} W (L - 2L_0) C_{ox} + W C_{ov}$$

$$C_{db} = C_{b0} W L_j + C_{sw} (2W + 2L_j)$$

$$L_j = 1.5 \mu m$$

$$C_{b0} = \frac{C_j}{(1 + \frac{V_R}{P_B}) M_J}$$

$$C_{sw} = \frac{C_{jsw}}{(1 + \frac{V_R}{P_B}) M_J s W}$$

$$V_g = (i_x + g_m V_{gs}) \left( R_s \parallel \frac{1}{s C_{gd}} \right)$$

$$= (i_x + g_m V_{gs}) \frac{R_s}{s R_s C_{gd} + 1}$$

$$V_{gs} = - (i_x + g_m V_{gs}) \frac{1}{s C_{gs}}$$

$$= - i_x \frac{1}{s C_{gs}} - g_m V_{gs} \frac{1}{s C_{gs}}$$

$$\left( 1 + \frac{g_m}{s C_{gs}} \right) V_{gs} = - i_x \frac{1}{s C_{gs}}$$

$$V_{gs} = \frac{- i_x}{s C_{gs} \left( 1 + \frac{g_m}{s C_{gs}} \right)} = - \frac{i_x}{s C_{gs} + g_m}$$

$$V_s = V_g - V_{gs}$$

$$= (i_x + g_m V_{gs}) \left( \frac{R_s}{s R_s C_{gd} + 1} - \frac{1}{s C_{gs}} \right)$$

$$= \left( 1 - \frac{1}{s C_{gs} + g_m} \right) i_x \left( \frac{R_s}{s R_s C_{gd} + 1} - \frac{1}{s C_{gs}} \right)$$

$$V_{DD} = 3V$$

$$C_{ox} = 3.9 \frac{\epsilon_o}{t_{ox}} = 3.83673 \times 10^{-7} F / cm^2$$

$$= 3.83673 \times 10^{-15} F / \mu m^2$$

$$\mu_n = 350 cm^2 / V \cdot s$$

$$V_{t_n} = 0.7$$

$$\mu_p = 100 cm^2 / V \cdot s$$

$$V_{t_p} = -0.8$$

$$k'_n = 0.13428 mA / V^2$$

$$k'_p = 0.03837 mA / V^2$$

$$C_{j_n} = 0.56 m$$

$$\lambda_n = 0.1$$

$$C_{j_p} = 0.99 m$$

$$\lambda_p = 0.2$$

$$L_{D_n} = 0.08 \mu$$

$$L_{D_p} = 0.09 \mu$$

$$V_x = \left( 1 - \frac{1}{sC_{gs} + g_m} \right) i_x \left( \frac{R_s}{sR_sC_{gd} + 1} - \frac{1}{sC_{gs}} \right) - (-i_x) \frac{1}{sC_{sb}}$$

$$= i_x \left[ \left( 1 - \frac{1}{sC_{gs} + g_m} \right) \left( \frac{R_s}{sR_sC_{gd} + 1} - \frac{1}{sC_{gs}} \right) + \frac{1}{sC_{sb}} \right]$$

$$\frac{V_x}{i_x} = R_{out} = \left( 1 - \frac{1}{sC_{gs} + g_m} \right) \left( \frac{R_s}{sR_sC_{gd} + 1} - \frac{1}{sC_{gs}} \right) + \frac{1}{sC_{sb}}$$

$$C_{ov} = 0.08 \mu m \cdot 3.83673 \times 10^{-15} \text{ F} / \mu m^2 = 306.9384 \times 10^{-18} \text{ F} / \mu m$$

$$C_{gs} = \frac{2}{3} \cdot 50 \mu m \cdot (0.5 \mu m - 2 \cdot 0.08 \mu m) \cdot 3.83673 \times 10^{-15} \text{ F} / \mu m^2 + 50 \mu m \cdot 306.9384 \times 10^{-18} \text{ F} / \mu m$$

$$= 58.8299 \text{ f}$$

$$C_{gd} = 0.4 \text{ nF} / m \times 50 \mu m$$

$$= 20 \text{ f}$$

$$k_1 = 0.13428 \text{ mA} / \text{V}^2 \times \frac{50 \mu m}{0.5 \mu m - 2 \times 0.08 \mu m}$$

$$= 19.74706 \text{ mA} / \text{V}^2$$

$$g_m = \sqrt{2 k I} = 6.28443 \text{ m}$$

$$R_s = 20 \text{ k}$$

After some simplification

$$R_{out} = \frac{R_s C_{gs} s + 1}{g_m + C_{gs} s}$$

When  $V_{in}$  is low freq.,  $s \rightarrow 0$

$$R_{out} \approx \frac{0 + 1}{g_m + 0} = \frac{1}{g_m} = 159.1233 \Omega$$

When  $V_{in}$  is high freq.,  $s \rightarrow \infty$

$$R_{out} \approx R_s = 20 \text{ k}$$

Inductive impedance has the form  $sL$ , and therefore increases with freq.


Capacitive impedance has the form  $\frac{1}{sC}$ , and therefore decreases with freq.

The output impedance of this circuit increases with freq. so it's inductive.

$$L = \frac{C_{gs}}{g_n} \left( R_s - \frac{1}{g_n} \right)$$

$$= 188.714 \text{ nH} \quad \#$$

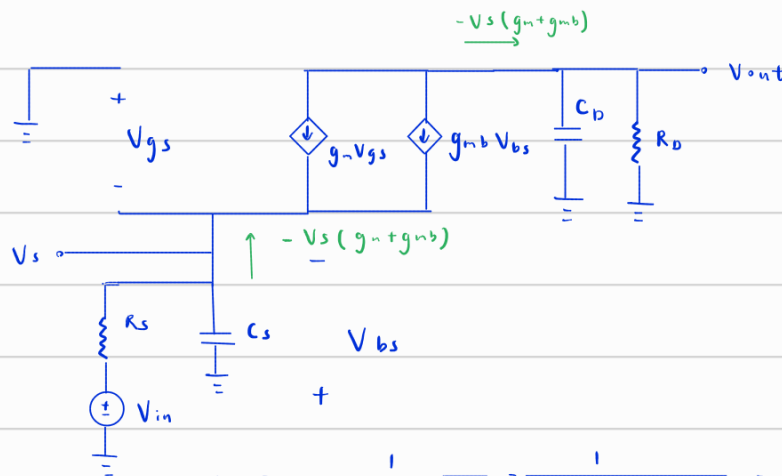4.2  $R_s = 1\text{k}$   $R_D = 2\text{k}$   $C_s = 101.2 \text{ fF}$   $C_D = 27.14 \text{ fF}$



$$W_{in} = \frac{1}{(R_s \parallel \frac{1}{g_n + g_{mb}}) C_s} = \frac{1}{138.5156 \cdot 101.2\text{f}} = 71.338 \text{ G rad/s} \quad \#$$

$$W_{out} = \frac{1}{C_D R_D} = \frac{1}{27.14\text{f} \cdot 2\text{k}} = 18.4230 \text{ G rad/s}$$

To determine low freq. gain, treat  $C_s$  &  $C_D$  as open circuit

$$A_v = \frac{R_D}{R_s + \frac{1}{g_n + g_{mb}}}$$

$$= 1.730 \text{ V/V} \quad \#$$

$$k = 0.13428 \text{ mA/V}^2 \times 100$$

$$= 13.428 \text{ mA/V}^2$$

$$\frac{1}{2} k (V_{gs} - 0.7)^2 = 1\text{m}$$

$$V_{gs} = \sqrt{\frac{2\text{m}}{k}} + 0.7$$

$$= 1.08593$$

$$1.45 - V_s = 1.08593$$

$$V_s = 0.36407 \text{ V} \quad V_{sb} = 0.36407$$

$$g_m = \sqrt{2kI}$$

$$= 5.1823 \text{ m}$$


$$g_{mb} = g_m \cdot \frac{\gamma}{2\sqrt{|2\phi_f + V_{sb}|}}$$

$$= 5.1823 \text{ m} \cdot \frac{0.95}{2\sqrt{|0.9 + 0.36407|}}$$

$$= 1.03710 \text{ m}$$

$$g_n + g_{mb} = 6.21940 \text{ m}$$

4.3

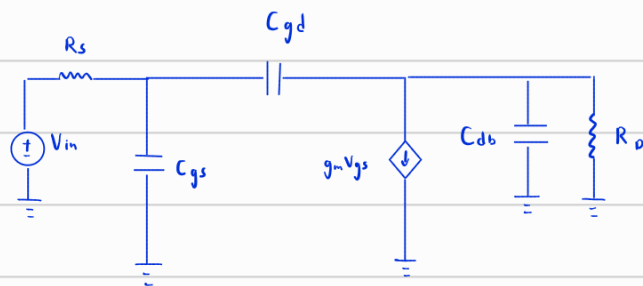

$$k = 0.13428 \text{ mA} / \text{V}^2 \times 100$$

$$R_s = 2 \text{ k}$$

$$= 13.428 \text{ mA} / \text{V}^2$$

$$R_D = 2 \text{ k}$$

$$g_m = 5.1823 \text{ m}$$

$$A_v = -g_m R_D$$

$$W_{in} = \frac{1}{R_s [C_{gs} + (1 + g_m R_D) C_{gd}]}$$

$$= -10.3646 \text{ V/V}$$

$$W_{out} = \frac{1}{R_D [C_{db} + (1 + \frac{1}{g_m R_D}) C_{gd}]}$$

$$C_{ov} = 0.08 \mu\text{m} \cdot 3.83673 \times 10^{-15} \text{ F} / \mu\text{m}^2 = 306.9384 \times 10^{-18} \text{ F} / \mu\text{m}$$

$$C_{gs} = 58.8299 \text{ f}$$

$$C_{gd} = 0.4 \text{ nF} / \text{m} \times 50 \mu\text{m}$$

$$= 20 \text{ f}$$

$$C_{bo} = \frac{C_j}{(1 + \frac{V_R}{P_B})^{MJ}}$$

$$C_j = 0.56 \text{ mF} / \text{m}^2$$

$$V_{DB} = 1 \text{ V}$$

$$P_B = 0.9$$

$$C_{sw} = \frac{C_{jsw}}{(1 + \frac{V_R}{P_B})^{MJsw}}$$

$$L_j = 1.5 \mu\text{m} \quad W = 50 \mu\text{m}$$

$$C_{jsw} = 3.5 \text{ pF} / \text{m}$$

$$C_{db} = C_{bo} W L_j + C_{sw} (2W + 2L_j)$$

$$MJ = 0.95$$

$$MJsw = 0.2$$

Exponents ☆

$$= \frac{C_j}{(1 + \frac{1}{P_B})^{MJ}} W L_j + \frac{C_{jsw}}{(1 + \frac{1}{P_B})^{MJsw}} (2W + 2L_j)$$

$$= \frac{0.56 \text{ m}}{(1 + \frac{1}{0.9})^{0.95}} 1.5 \mu 50 \mu + \frac{3.5 \text{ p}}{(1 + \frac{1}{0.9})^{0.2}} (100 \mu + 3 \mu)$$

$$= 30.31723 \text{ fF}$$

$$\omega_{in} = \frac{1}{R_s [C_{gs} + (1 + g_m R_o) C_{gd}]} = 1.748 \text{ G rad/s} \quad \#$$

$$\omega_{out} = \frac{1}{R_o [C_{db} + (1 + \frac{1}{g_m R_o}) C_{gd}]} = 9.570 \text{ G rad/s} \quad \#$$

$$\omega_z = \frac{g_m}{C_{gd}} = 259.115 \text{ G rad/s} \quad \#$$