

AIC HW5

111511076 陳彥宇

Problem 1:

NO.	Performance Parameters	TT	FF	SS	FnSp	SnFp
1	DC Gain(dB)	71.9366	68.9745	72.8455	70.8103	72.7023
2	3-dB Bandwidth(Hz)	4.2395k	6.0042k	3.7281k	4.8376k	3.8657k
3	Slew Rate(V/us)	17.8	17.9	16.9	17.4	18
4	Settling Time(us)	0.68	0.78	0.62	0.69	0.53
5	CMRR(dB)	210.7917	202.7448	214.8733	206.5053	206.3872
6	PSRR(VDD)(dB)	209.5586	226.8923	209.6000	222.4707	204.4728
7	PSRR(GND)(dB)	221.7783	225.2085	216.3918	219.7673	235.7218
8	Unity-gain Frequency(Hz)	16.2195M	16.3384M	15.8460M	16.2718M	16.1411M
9	Phase Margin (°)	74.2417	73.9909	74.5330	74.3321	74.1580
10	Power(uW)	467.9814	468.3307	467.4536	467.7367	468.1831

 


Fig 1. TT Bode Plot (DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)



Fig 2. TT Slew Rate & Settling Time

```
***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgaindb= 71.9366      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
dcgainv/v= 3.9521k    at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
f3db= 4.2395k
funity= 16.2195x
wgc_phase=-105.7583
pm= 74.2417
*****
```

Fig 3. TT .measure(DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)

```
****      small-signal transfer characteristics
| |      v(vout+,vout-)/v_common      = -114.0888n
| |      input resistance at          v_common = 1.000e+20
| |      output resistance at v(vout+,vout-)      = 14.4535x
```

Fig 4. TT .measure(Common-mode Gain)

```

****      small-signal transfer characteristics

v(vout+,vout-)/vsupply      = 131.4910n
input resistance at          vsupply = 320.2773k
output resistance at v(vout+,vout-) = 14.4535x

```

Fig 5. TT .measure(Gain from VDD)

```

****      small-signal transfer characteristics

v(vout+,vout-)/vss          = 32.2041n
input resistance at          vss  = -2.545e+13
output resistance at v(vout+,vout-) = 14.4535x

```

Fig 6. TT .measure(Gain from GND)

```

**** voltage sources

subckt
element 0:v1      0:v2      0:v3      0:v_common 0:vss      0:vsupply
volts    800.0000m 800.0000m 900.0000m 0.         0.         1.8000
current  0.        0.        0.        0.         58.7860f -259.9897u
power    0.        0.        0.        0.         0.         467.9814u

total voltage source power dissipation= 467.9814u      watts

```

Fig 7. TT Power

 


Fig 8. FF Bode Plot (DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)



Fig 9. FF Slew Rate & Settling Time

```

***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgaindb= 68.9745      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
dcgainv/v= 2.8101k      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
f3db= 6.0042k
funity= 16.3384x
wgc_phase=-106.0091
pm= 73.9909
*****

```

Fig 10. FF .measure(DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)

```

****      small-signal transfer characteristics
| | | | | v(vout+,vout-)/v_common      = 204.8710n
| | | | | input resistance at          v_common = 1.000e+20
| | | | | output resistance at v(vout+,vout-)      = 10.2242x

```

Fig 11. FF .measure(Common-mode Gain)

```

****      small-signal transfer characteristics
| | | | | v(vout+,vout-)/vsupply      = 12.7088n
| | | | | input resistance at          vsupply = 673.1213k
| | | | | output resistance at v(vout+,vout-)      = 10.2242x

```

Fig 12. FF .measure(Gain from VDD)

```

****      small-signal transfer characteristics
| | | | | v(vout+,vout-)/vss      = 15.4276n
| | | | | input resistance at          vss      = -1.272e+13
| | | | | output resistance at v(vout+,vout-)      = 10.2242x

```

Fig 13. FF .measure(Gain from GND)

```

**** voltage sources

subckt
element 0:v1      0:v2      0:v3      0:v_common 0:vss      0:vsupply
volts    800.0000m  800.0000m  900.0000m   0.         0.         1.8000
current  0.         0.         0.         0.         29.7816f  -260.1837u
power    0.         0.         0.         0.         0.         468.3307u

total voltage source power dissipation= 468.3307u      watts

```

Fig 14. FF Power

 


Fig 15. SS Bode Plot (DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)



Fig 16. SS Slew Rate & Settling Time

```

***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgaindb= 72.8455      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
dcgainv/v= 4.3881k     at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
f3db= 3.7281k
funity= 15.8460x
wgc_phase=-105.4670
pm= 74.5330
*****

```

Fig 17. SS .measure(DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)

```

****      small-signal transfer characteristics

| | | | | v(vout+,vout-)/v_common      = -79.1793n
| | | | | input resistance at          v_common = 1.000e+20
| | | | | output resistance at v(vout+,vout-)    = 16.4022x

```

Fig 18. SS .measure(Common-mode Gain)

```

****      small-signal transfer characteristics

| | | | | v(vout+,vout-)/vsupply      = 145.3043n
| | | | | input resistance at          vsupply = 146.3439k
| | | | | output resistance at v(vout+,vout-)    = 16.4022x

```

Fig 19. SS .measure(Gain from VDD)

```

****      small-signal transfer characteristics

| | | | | v(vout+,vout-)/vss      = -66.4796n
| | | | | input resistance at          vss      = -1.043e+13
| | | | | output resistance at v(vout+,vout-)    = 16.4022x

```

Fig 20. SS .measure(Gain from GND)


```

*** voltage sources

subckt
element  0:v1      0:v2      0:v3      0:v_common 0:vss      0:vsupply
volts    800.0000m 800.0000m 900.0000m  0.        0.        1.8000
current  0.        0.        0.        0.        93.9871f -259.6965u
power    0.        0.        0.        0.        0.        467.4536u

total voltage source power dissipation= 467.4536u      watts

```

Fig 21. SS Power

 


Fig 22. FnSp Bode Plot (DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)



Fig 23. FnSp Slew Rate & Settling Time

```

***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgaindb= 70.8103      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
dcgainv/v= 3.4715k    at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
f3db= 4.8376k
funity= 16.2718x
wgc_phase=-105.6679
pm= 74.3321
*****

```

Fig 24. FnSp .measure(DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)

```

****      small-signal transfer characteristics
| |      v(vout+,vout-)/v_common      = -164.1548n
| |      input resistance at          v_common = 1.000e+20
| |      output resistance at v(vout+,vout-) = 12.6682x

```

Fig 25. FnSp TT .measure(Common-mode Gain)

```

****      small-signal transfer characteristics
| |      v(vout+,vout-)/vsupply      = -26.1205n
| |      input resistance at          vsupply = 216.5334k
| |      output resistance at v(vout+,vout-) = 12.6682x

```

Fig 26. FnSp TT .measure(Gain from VDD)

```

****      small-signal transfer characteristics
| |      v(vout+,vout-)/vss      = -35.6574n
| |      input resistance at          vss = -5.647e+13
| |      output resistance at v(vout+,vout-) = 12.6682x

```

Fig 27. FnSp TT .measure(Gain from GND)

```

*** voltage sources

subckt
element  0:v1      0:v2      0:v3      0:v_common 0:vss      0:vsupply
volts    800.0000m 800.0000m 900.0000m 0.         0.         1.8000
current  0.        0.        0.        0.        -5.6399f -259.8537u
power    0.        0.        0.        0.        0.         467.7367u

total voltage source power dissipation= 467.7367u watts

```

Fig 28. FnSp Power

 


Fig 29. SnFp Bode Plot (DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)

 


Fig 30. SnFp Slew Rate & Settling Time

```

***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgaindb= 72.7023      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
dcgainv/v= 4.3163k      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
f3db= 3.8657k
funity= 16.1411x
wgc_phase=-105.8420
pm= 74.1580
*****

```

Fig 31. SnFp .measure(DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)

```

****      small-signal transfer characteristics

| | | | | v(vout+,vout-)/v_common      = -206.8962n
| | | | | input resistance at          v_common = 1.000e+20
| | | | | output resistance at v(vout+,vout-)      = 15.8476x

```

Fig 32. SnFp .measure(Common-mode Gain)

```

****      small-signal transfer characteristics

| | | | | v(vout+,vout-)/vsupply      = -257.9120n
| | | | | input resistance at          vsupply = 485.3339k
| | | | | output resistance at v(vout+,vout-)      = 15.8476x

```

Fig 33. SnFp .measure(Gain from VDD)

```

****      small-signal transfer characteristics

| | | | | v(vout+,vout-)/vss      = 7.0635n
| | | | | input resistance at          vss = -1.100e+14
| | | | | output resistance at v(vout+,vout-)      = 15.8476x

```

Fig 34. SnFp .measure(Gain from GND)

```

**** voltage sources

subckt
element 0:v1      0:v2      0:v3      0:v_common 0:vss      0:vsupply
volts    800.0000m  800.0000m  900.0000m  0.          0.          1.8000
current  0.          0.          0.          0.          93.9871f -259.6965u
power    0.          0.          0.          0.          0.          467.4536u

total voltage source power dissipation= 467.4536u      watts

```

Fig 35. SnFp Power

Problem 2:

 


Fig 36. M2 W/L = 60.1u/4u TT Bode Plot (DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)



Fig 37. M2 W/L = 60.1u/4u TT Slew Rate & Settling Time

```
***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgaindb= 59.1438      at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
dcgainv/v= 906.1296    at= 1.0000
| | | | | from= 1.0000      to= 501.1872x
f3db= 18.2747k
funity= 16.0809x
wgc_phase=-105.5453
pm= 74.4547
*****
```

Fig 38. M2 W/L = 60.1u/4u TT .measure(DC Gain, Bandwidth, Unity-gain Freq., Phase Margin)

```
****      small-signal transfer characteristics
| |      v(vout+,vout-)/v_common      = 404.2798m
| |      input resistance at          v_common = 1.000e+20
| |      output resistance at v(vout+,vout-)      = 3.3135x
```

Fig 39. M2 W/L = 60.1u/4u TT .measure(Common-mode Gain)

```

****      small-signal transfer characteristics

v(vout+,vout-)/vsupply      =   -1.3063
input resistance at          vsupply =   218.2254k
output resistance at v(vout+,vout-) =    3.3135x

```

Fig 40. M2 W/L = 60.1u/4u TT .measure(Gain from VDD)

```

****      small-signal transfer characteristics

v(vout+,vout-)/vss          =    3.2729n
input resistance at          vss  =  -1.720e+13
output resistance at v(vout+,vout-) =    3.3135x

```

Fig 41. M2 W/L = 60.1u/4u TT .measure(Gain from GND)

```

**** voltage sources

subckt
element  0:v1      0:v2      0:v3      0:v_common 0:vss      0:vsupply
volts    800.0000m  800.0000m  900.0000m  0.         0.         1.8000
current  0.         0.         0.         0.         39.9102f  -260.0234u
power    0.         0.         0.         0.         0.         468.0421u

total voltage source power dissipation= 468.0421u      watts

```

Fig 42. M2 W/L = 60.1u/4u TT .measure(Power)

NO.	Performance Parameters	TT M2 W/L = 60.1u/4u	TT M2 W/L = 60u/4u
1	DC Gain(dB)	59.1438	71.9366
2	3-dB Bandwidth(Hz)	18.2747k	4.2395k
3	Slew Rate(V/us)	17.8	17.8
4	Settling Time(us)	0.68	0.68
5	CMRR(dB)	67.0102	210.7917
6	PSRR(VDD)(dB)	56.8229	209.5586
7	PSRR(GND)(dB)	228.8452	221.7783
8	Unity-gain	16.0809M	16.2195M

	Frequency(Hz)		
9	Phase Margin (°)	74.4547	74.2417
10	Power(uW)	468.0421	467.9814

 


Fig 43. M2 W/L = 60.1u/4u & M2 W/L = 60u/4u TT Bode Plot Comparison

Comparison & Discussion:

Because the widths of the MOSFETs in the differential amplifier are mismatched, it causes imbalance in the differential pair, leading to several undesirable effects:

1. Mismatch in Transconductance (gm)

The transconductance g_m of a MOSFET depends on its width (W). Because the width are mismatched, the g_m values of the two sides are different. This results in an unequal current flow in the differential branches, even when the input voltages are balanced. This imbalance reduces the symmetry of the circuit and affects the differential amplifier's performance.

2. Reduced Common-Mode Rejection Ratio (CMRR)

The differential amplifier is designed to amplify differential signals and reject common-mode signals. As we can see from the .tf results above, the mismatched widths degrade the common-mode rejection ratio (CMRR) because

the differential pair no longer perfectly cancels common-mode signals.

3. Reduced Power Supply Rejection Ratio (PSRR)

The same reasons CMRR is reduced can be applied here. Unequal g_m makes the amplifier more sensitive to variations in the power supply.

4. Reduced Gain and Linearity

The differential gain of the amplifier depends on the matching of the transistors. Width mismatch has reduced the gain and affected the linearity of the amplifier. Its gain reduced by approximately 12.8dB compared to the perfectly matched amplifier.

5. Phase Response

The width of a MOSFET directly influences its parasitic capacitances. Therefore, the first pole of the mismatched amplifier is shifted to the right by approximately 15.7Hz.

6. Slew Rate & Settling Time

The slew rate and settling time seem to be unaffected by the mismatch.

Code for Problems 1 & 2:

```
1. ***-----***
2. ***      setting      ***
3. ***-----***
4. .lib "~/U18_HSPICE_Model/mm180_reg18_v124.lib" tt
5. .TEMP 25
6. .op 0.5m
7. ***-----***
8. ***      simulation      ***
9. ***-----***
10.
11. .option post
12. .option accurate=1
13. .ac DEC 100 1 500Meg
14. .probe AC P(Vout+,Vout-)
15. .probe AC Vdb(Vout+,Vout-)
```

```

16. .probe AC VP(Vout+,Vout-)
17. .tran 0.1n 20u
18. .probe tran V(Vout+, Vout-)
19. .tf V(Vout+, Vout-) V1
20.
21. ***-----***
22. ***      measure      ***
23. ***-----***
24. .meas AC DCgainDB max Vdb(Vout+,Vout-)
25. .meas AC DCgainV/V max V(Vout+,Vout-)
26. .meas AC f3db when Vdb(Vout+,Vout-)= 'DCgainDB-3.0'
27. .meas AC funity when Vdb(Vout+,Vout-)= '0'
28. .meas AC wgc_phase find VP(Vout+,Vout-) when Vdb(Vout+,Vout-)= '0'
29. .meas AC PM param = 'wgc_phase + 180'
30. .meas tran avg_power avg power
31.
32. .meas tran vout_max param = '1.25'
33. .meas tran delta_t trig V(Vout+,Vout-) val='1.25*0.1' rise = 1
34. +targ V(Vout+,Vout-) val='1.25*0.9' rise = 1
35. .meas tran slew_rate param = "(1.25*0.9 - 1.25*0.1) / delta_t"
36.
37. ***-----***
38. ***      power/input      ***
39. ***-----***
40. Vsupply      VDD      vss      1.8V
41. V1           Vin+     Common    DC      0.8V      AC 0.5V 0
42. V2           Vin-     Common    DC      0.8V      AC 0.5V 180
43. V_common     Common    vss      DC      0V
44. Vgnd         GND 0 0V
45. VSS          vss GND 0V
46.
47. V3 Vcmo      vss 0.9V
48. I1 VDD       Vb2 50uA
49. I2 Vb3       vss 50uA
50. I3 Vb4       vss 50uA
51.
52. ***-----***
53. ***      circuit      ***

```

```

54. ***-----***
55. Mb1      Vb2      Vb2      vss      vss      n_18_mm w=3u   l=4u      ad=0.48u*3u
as=0.48u*3u pd=0.96u+3u ps=0.96u+3u
56. Mb2      Vb3      Vb3      VDD      VDD      p_18_mm w=15u  l=4u      ad=0.48u*15u
as=0.48u*15u pd=0.96u+15u ps=0.96u+15u
57. Mb3      N1       Vb4      VDD      VDD      p_18_mm w=90u  l=4u      ad=0.48u*90u
as=0.48u*90u pd=0.96u+90u ps=0.96u+90u
58. Mb4      Vb4      Vb3      N1       VDD      p_18_mm w=50u  l=4u      ad=0.48u*50u
as=0.48u*50u pd=0.96u+50u ps=0.96u+50u
59.
60. MSS      N2       Vb1      vss      vss      n_18_mm w=150u l=8u      ad=0.48u*150u
as=0.48u*150u pd=0.96u+150u ps=0.96u+150u
61. M1       N3       Vin+     N2       vss      n_18_mm w=60u  l=4u      ad=0.48u*60u
as=0.48u*60u pd=0.96u+60u ps=0.96u+60u
62. M2       N4       Vin-     N2       vss      n_18_mm w=60u  l=4u      ad=0.48u*60u
as=0.48u*60u pd=0.96u+60u ps=0.96u+60u
63. M3       Vout-     Vb2      N3       vss      n_18_mm w=65u  l=4u      ad=0.48u*65u
as=0.48u*65u pd=0.96u+65u ps=0.96u+65u
64. M4       Vout+     Vb2      N4       vss      n_18_mm w=65u  l=4u      ad=0.48u*65u
as=0.48u*65u pd=0.96u+65u ps=0.96u+65u
65.
66. CL1      Vout-     vss      5p
67. CL2      Vout+     vss      5p
68.
69. M5       Vout-     Vb3      N5       VDD      p_18_mm w=50u  l=4u      ad=0.48u*50u
as=0.48u*50u pd=0.96u+50u ps=0.96u+50u
70. M6       Vout+     Vb3      N6       VDD      p_18_mm w=50u  l=4u      ad=0.48u*50u
as=0.48u*50u pd=0.96u+50u ps=0.96u+50u
71. M7       N5       Vb4      VDD      VDD      p_18_mm w=90u  l=4u      ad=0.48u*90u
as=0.48u*90u pd=0.96u+90u ps=0.96u+90u
72. M8       N6       Vb4      VDD      VDD      p_18_mm w=90u  l=4u      ad=0.48u*90u
as=0.48u*90u pd=0.96u+90u ps=0.96u+90u
73.
74. M9       Vb1      Vb1      vss      vss      n_18_mm w=8u   l=8u      ad=0.48u*8u
as=0.48u*8u pd=0.96u+8u ps=0.96u+8u
75. M10      N7       N7       vss      vss      n_18_mm w=8u   l=8u      ad=0.48u*8u
as=0.48u*8u pd=0.96u+8u ps=0.96u+8u

```

```

76. M11      N7      Vout-  N8      N8      p_18_mm w=5u  l=1u  ad=0.48u*5u
as=0.48u*5u pd=0.96u+5u ps=0.96u+5u
77. M12      Vb1      Vcmo   N8      N8      p_18_mm w=5u  l=1u  ad=0.48u*5u
as=0.48u*5u pd=0.96u+5u ps=0.96u+5u
78. M13      Vb1      Vcmo   N9      N9      p_18_mm w=5u  l=1u  ad=0.48u*5u
as=0.48u*5u pd=0.96u+5u ps=0.96u+5u
79. M14      N7      Vout+  N9      N9      p_18_mm w=5u  l=1u  ad=0.48u*5u
as=0.48u*5u pd=0.96u+5u ps=0.96u+5u
80. M15      N8      Vb4      VDD     VDD     p_18_mm w=9u  l=4u  ad=0.48u*9u
as=0.48u*9u pd=0.96u+9u ps=0.96u+9u
81. M16      N9      Vb4      VDD     VDD     p_18_mm w=9u  l=4u  ad=0.48u*9u
as=0.48u*9u pd=0.96u+9u ps=0.96u+9u
82.
83. *Original circuit measures DC gain, 3-dB bandwidth, power, unity gain freq., Phase
Margin
84.
85. .alter
86. *measures Acm
87. .tf V(Vout+, Vout-) V_common
88. V1      Vin+    Common  DC      0.8V
89. V2      Vin-    Common  DC      0.8V
90. V_common Common  vss    DC      0V      AC 0.5
91.
92. .alter
93. *measures Slew Rate, Settling Time
94. *
PULSE(V1 V2 Tdelay Trise Tfall Pwidth Period)
95. V1      Vin+    vss    PULSE(0V 1.8V 1us 0ns 0ns 30us 50us)
96. V2      Vin-    vss    DC      0.8V
97. V_common Common  vss    DC      0V
98.
99. .alter
100. *measures gain from GND
101. .tf V(Vout+, Vout-) VSS
102. V_common Common  vss    DC      0V
103. VSS      vss      GND    DC      0V      AC 1
104.
105. .alter
106. *measures gain from VDD

```

```
107. .tf V(Vout+, Vout-) Vsupply
108. V_common Common vss DC 0V
109. VSS vss GND DC 0V
110. Vsupply VDD vss DC 1.8V AC 1
111.
112. .end
```