

AIC HW4

Name: 陳彥宇 ID: 111511076

Problem 1

	Fig.(a)	Fig.(b)	Fig.(c)
Av(dB)	17.9287	0.06003	18.0703
3-dB bandwidth (Hz)	90.622M	229.905M	117.372M

```
***** ac analysis tnom= 25.000 temp= 25.000 *****
gain_a= 7.8784
gain_b= 1.0069
gain_c= 8.0079

***** job concluded
```

Fig. 1: Low-Frequency Gain .measure Result

```
***** ac analysis tnom= 25.000 temp= 25.000 *****
a_gainmax= 17.9287 at= 2.4547
from= 1.0000 to=1000.0000x
a_f3db= 90.6221x
b_gainmax= 60.0300m at= 6.3096
from= 1.0000 to=1000.0000x
b_f3db= 229.9052x
c_gainmax= 18.0703 at= 3.1623
from= 1.0000 to=1000.0000x
c_f3db= 117.3718x

***** job concluded
```

Fig. 2: -3dB Gain

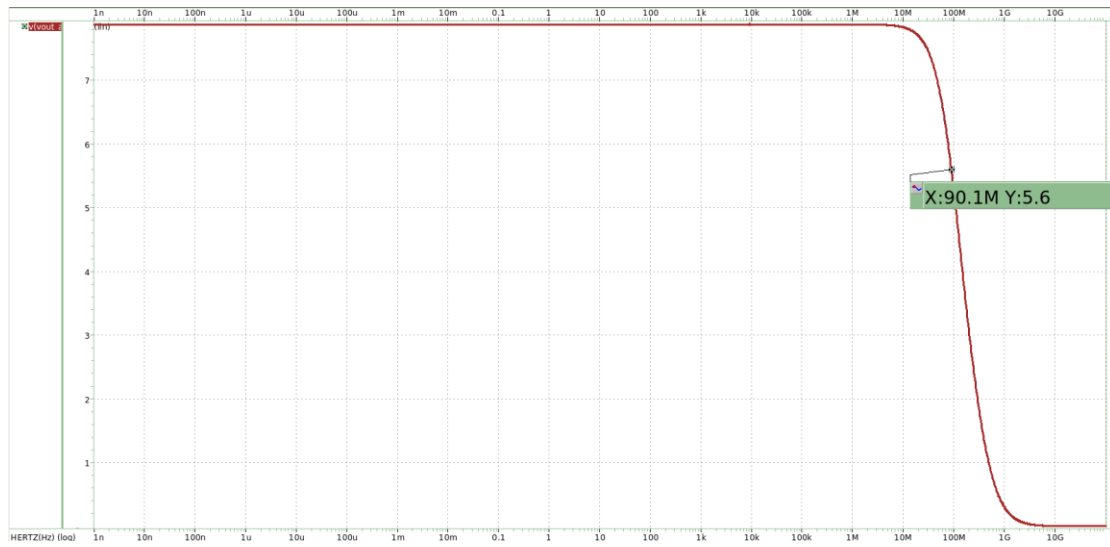


Fig. 3: Circuit (a) -3dB Freq.



Fig. 4: Circuit (b) -3dB Freq.



Fig. 5: Circuit (c) -3dB Freq.

Problem 1 Code

```

1. ***-----***
2. ***      setting      ***
3. ***-----***
4. .lib "~/U18_HSPICE_Model/mm180_reg18_v124.lib" tt
5. .TEMP 25
6. .op
7. ***-----***
8. ***      simulation      ***
9. ***-----***
10.
11. .option post
12. .AC DEC 100 1n 100G
13.
14. ***-----***
15. ***      parameters      ***
16. ***-----***
17. .global VDD GND
18. ***-----***
19. ***      measure      ***

```

```

20. ***-----***
21. .measure ac Gain_a      FIND V(VOUT_a) at=10000Hz
22. .measure ac Gain_b      FIND V(VOUT_b) at=10000Hz
23. .measure ac Gain_c      FIND V(VOUT_c) at=10000Hz
24.
25. ***-----***
26. ***      power/input      ***
27. ***-----***
28. Vsupply VDD GND 1.8V
29.
30. ***-----***
31. ***      circuit      ***
32. ***-----***
33.
34. Xa VIN_a VOUT_a CKT_A
35. Xb VIN_b VOUT_b CKT_B
36. Xc VIN_c VOUT_c CKT_C
37.
38. .subckt CKT_A VIN VOUT
39. RD VDD VOUT 15k
40. RS VIN Gate 10k
41. MN VOUT Gate GND GND n_18_mm w=13u l=1.3u
42. C1 VOUT GND 0.02p
43. V1 VIN GND DC 0.6V AC 1
44. .ends
45.
46. .subckt CKT_B VIN VOUT
47. RD VDD VOUT 15k
48. RS VIN Source 10k
49. MN VOUT Vb Source GND n_18_mm w=13u l=1.3u
50. C1 VOUT GND 0.02p
51. V1 VIN GND DC 0.3V AC 1
52. V2 Vb GND DC 0.9V
53. .ends
54.
55. .subckt CKT_C VIN VOUT
56. RD VDD VOUT 15k
57. RS VIN G1 10k

```

```

58. MN2 VOUT Vb VX VX n_18_mm w=13u l=1.3u
59. MN1 VX G1 GND GND n_18_mm w=13u l=1.3u
60. C1 VOUT GND 0.02p
61. V1 VIN GND DC 0.6V AC 1
62. V3 Vb GND 0.9V
63. .ends
64.
65. .end

```

Problem 2:

Compare both low-frequency voltage gain A_v and 3-dB bandwidth between these two amplifiers in Figs. (a) and (b). Please explain the reasons why they are larger or smaller.

Circuit (a) is a CS amplifier. Because the gate oxide is SiO₂ (basically glass), its input resistance looking into the gate is very high. On the other hand, circuit (b) is a CG amplifier, the input resistance looking into the source is given by $1/g_m$. $1/g_m$ is typically only $1 \sim 2\text{k}\Omega$. After voltage division with R_s ($10\text{k}\Omega$), the input voltage is significantly reduced to less than 20% its original value. This is why even though circuit (a) & (b) have identical output resistance, but (b) has a lower gain. This low input resistance problem can be resolved by using a cascode amplifier, as shown in circuit (c).

While CS amplifiers have the advantage of high input resistance, they have the problem of small bandwidth due to Miller effect. Due to this, the input capacitance is greatly increased, as shown by the following equation:

$$C_{in} \approx C_{gd} \times (1 + |A_v|)$$

CG amplifiers do not experience Miller effect, so they have a larger gain bandwidth. As shown in problem 1, the CS amplifier of circuit (a) only has a bandwidth of 90.1MHz, while the CG amplifier of circuit (b) has a bandwidth of 231MHz. We can combine the best of both worlds: high input resistance & large bandwidth by using a cascode amplifier, like the one in circuit (c).

Problem 3:

Compare both output noise voltage and input-referred noise between these two amplifiers in Figs. (a) and (c). Please describe the results you observed and explain whether you think MN2 in Fig. (c) has a significant impact on the total output noise. If not, please explain the reason for your assessment.

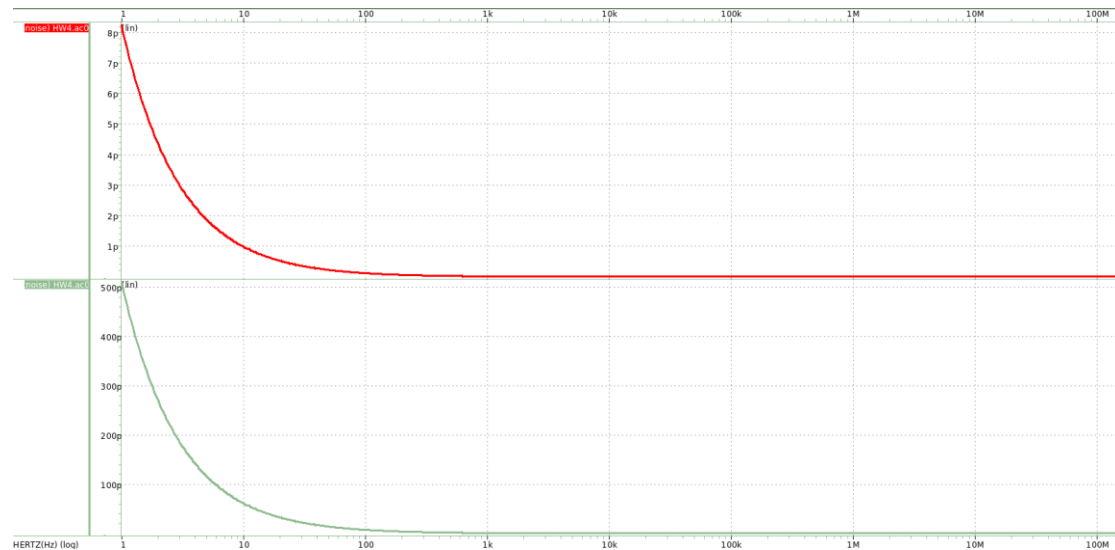


Fig. 6: Circuit (a) innoise & outnoise 1 ~ 150MHz

```
**** the results of the sqrt of integral (V^2 / freq)
      from fstart upto 151.3561x      Hz. using more freq points
      results in more accurate total noise values.

**** total output noise voltage   =   1.0794m      V

**** total equivalent input noise = 175.3984u      V
```

Fig. 7: Circuit (a) Input-referred Noise

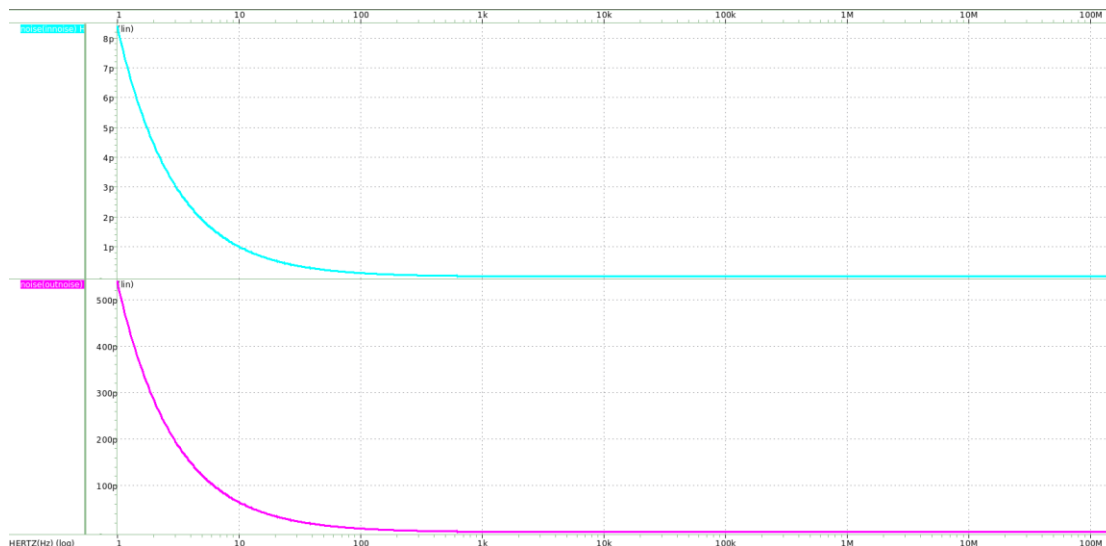


Fig. 8: Circuit (c) innoise & outnoise 1 ~ 150MHz

```

**** the results of the sqrt of integral (V^2 / freq)
      from fstart upto 151.3561x      Hz. using more freq points
      results in more accurate total noise values.

**** total output noise voltage  =  1.1921m      V

**** total equivalent input noise = 177.6834u      V

```

Fig. 9: Circuit (c) Input-referred Noise

MN2 of circuit(c) has very small impact on the total output noise at low frequencies. We can use the following equivalent circuit to analyze this:

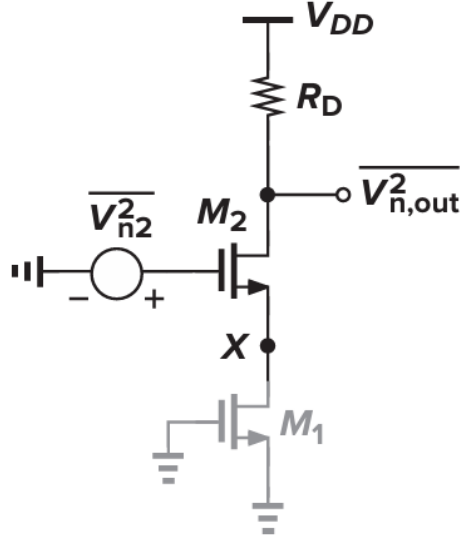


Fig. 10: Equivalent Circuit for M2 Input-referred Noise

In this circuit, the input-referred noise of M2 passes through a source-degenerated CS configuration, whose G_m is given by:

$$G_{m2} = \frac{g_{m2}}{1 + g_{m2}R_x}$$

The equation indicates that the gain seen from the M2's gate to M2's drain is small if R_x is large. In order to prove this through simulation, I modified my code to run an AC analysis from M2's gate to M2's drain. Notice that the gain at low frequency is quite small. However, the gain begins to increase past 10MHz. This is due to the capacitance at node X. At high frequencies, the gain from M2's gate to M2's drain is given by:

$$\frac{V_{n,out}}{V_{n2}} \approx \frac{-R_D}{\frac{1}{g_{m2}} + \frac{1}{C_x s}}$$

Therefore, M2 starts contributing more to the total output noise as the frequency increases.

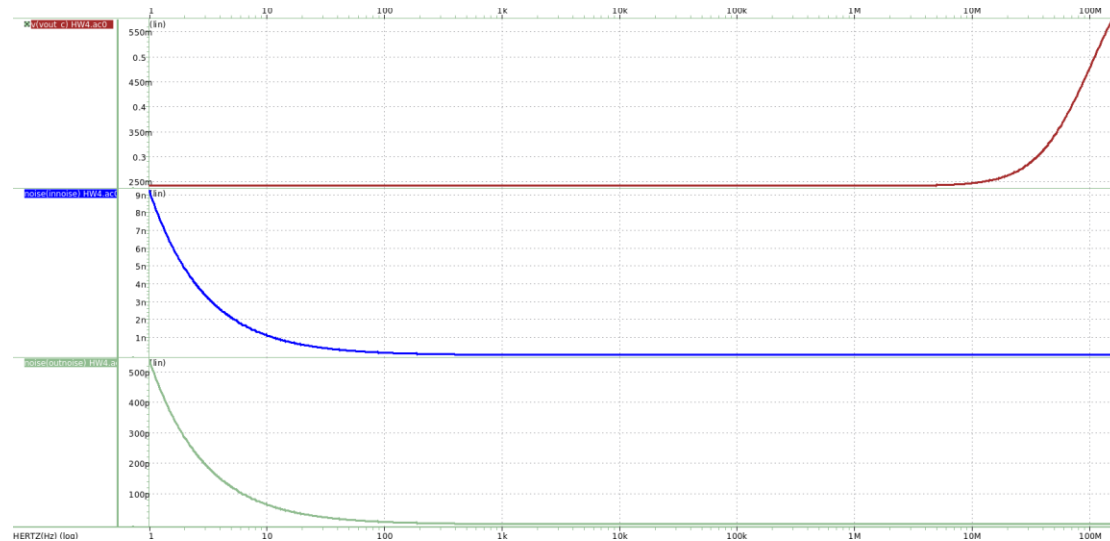


Fig. 11: Circuit (c) innoise & outnoise 1 ~ 150MHz from M2's gate to M2's drain

Problem 3 Code:

```

1. ***-----***
2. ***      setting      ***
3. ***-----***
4. .lib "~\U18_HSPICE_Model\mm180_reg18_v124.lib" tt
5. .TEMP 25
6. .op
7. ***-----***
8. ***      simulation      ***
9. ***-----***
10.
11. .option post
12. .ac DEC 100 1 150Meg
13. .noise V(VOUT_a) VA 1
14.
15. ***-----***
16. ***      parameters      ***
17. ***-----***
18. .global VDD GND
19. ***-----***

```

```

20. ***          measure          ***
21. ***-----***
22.
23. ***-----***
24. ***          power/input      ***
25. ***-----***
26. Vsupply VDD GND 1.8V
27. VA VIN_a    GND   DC    0.6V    AC  1
28. VC VIN_c    GND   DC    0.6V    AC  1
29.
30. ***-----***
31. ***          circuit          ***
32. ***-----***
33. Xa VIN_a    VOUT_a CKT_A
34. Xc VIN_c    VOUT_c CKT_C
35.
36. .subckt CKT_A VIN    VOUT
37. RD VDD      VOUT  15k
38. RS VIN      Gate  10k
39. MN VOUT     Gate  GND    GND    n_18_mm w=13u l=1.3u
40. C1 VOUT     GND   0.02p
41. *V1 VIN     GND   DC    0.6V    AC  1
42. .ends
43.
44. .subckt CKT_B VIN    VOUT
45. RD VDD      VOUT  15k
46. RS VIN      Source 10k
47. MN VOUT     Vb     Source GND    n_18_mm w=13u l=1.3u
48. C1 VOUT     GND   0.02p
49. V1 VIN     GND   DC    0.3V    AC  1
50. V2 Vb      GND   DC    0.9V
51. .ends
52.
53. .subckt CKT_C VIN    VOUT
54. RD VDD      VOUT  15k
55. RS VIN     G1    10k
56. MN2 VOUT   Vb    VX     VX     n_18_mm w=13u l=1.3u
57. MN1 VX     G1    GND    GND    n_18_mm w=13u l=1.3u

```

```
58. C1 VOUT GND 0.02p
59. V3 Vb GND 0.9V
60. .ends
61.
62. .alter
63. .noise V(VOUT_c) VC 1
64.
65. .end
66.
```