

Homework #6 of 「類比積體電路導論」

作業繳交截止日期: **Nov. 28, 2024 12:00** (上傳 **E3 數位平台** 繳交)

本次作業共三大題, 6.1~6.3

請將作業轉成一個 PDF 檔案(file size 小於 10MB), 檔名請使用

「AIC_HW6_自己的學號」(例如: AIC_HW6_109700018), 於作業繳

交截止日期/時間前, 上傳到指定的 **E3 數位平台** 繳交。

Unless otherwise stated, in the following problems, use the device data shown in Table 1 and assume that $V_{DD} = 3V$. The Dielectric constant of gate oxide is 3.9 and $\epsilon_o = 8.854 \times 10^{-12} F/m$.

NMOS Model			
LEVEL = 1	VTO = 0.7	GAMMA = 0.45	PHI = 0.9
NSUB = 9e+14	LD = 0.08e-6	UO = 350	LAMBDA = 0.1
TOX = 9e-9	PB = 0.9	CJ = 0.56e-3	CJSW = 0.35e-11
MJ = 0.45	MJSW = 0.2	CGDO = 0.4e-9	JS = 1.0e-8
PMOS Model			
LEVEL = 1	VTO = -0.8	GAMMA = 0.4	PHI = 0.8
NSUB = 5e+14	LD = 0.09e-6	UO = 100	LAMBDA = 0.2
TOX = 9e-9	PB = 0.9	CJ = 0.94e-3	CJSW = 0.32e-11
MJ = 0.5	MJSW = 0.3	CGDO = 0.3e-9	JS = 0.5e-8

VTO: threshold voltage with zero V_{SB} (unit: V)

GAMMA: body-effect coefficient (unit: $V^{1/2}$)

PHI: $2\Phi_F$ (unit: V)

TOX: gate-oxide thickness (unit: m)

NSUB: substrate doping (unit: cm^{-3})

LD: source/drain side diffusion (unit: m)

UO: channel mobility (unit: $cm^2/V/s$)

LAMBDA: channel-length modulation coefficient (unit: V^{-1})

CJ: source/drain bottom-plate junction capacitance per unit area (unit: F/m^2)

CJSW: source/drain sidewall junction capacitance per unit length (unit: F/m)

PB: source/drain junction built-in potential (unit: V)

MJ: exponent in CJ equation (unitless)

MJSW: exponent in CJSW equation (unitless)

CGDO: gate-drain overlap capacitance per unit width (unit: F/m)

CGSO: gate-source overlap capacitance per unit width (unit: F/m)

JS: source/drain leakage current per unit area (unit: A/m^2)

6.1 Using feedback techniques, calculate the input and output impedances of each circuit at relatively low frequencies in Fig 1. Neglecting channel length modulation.

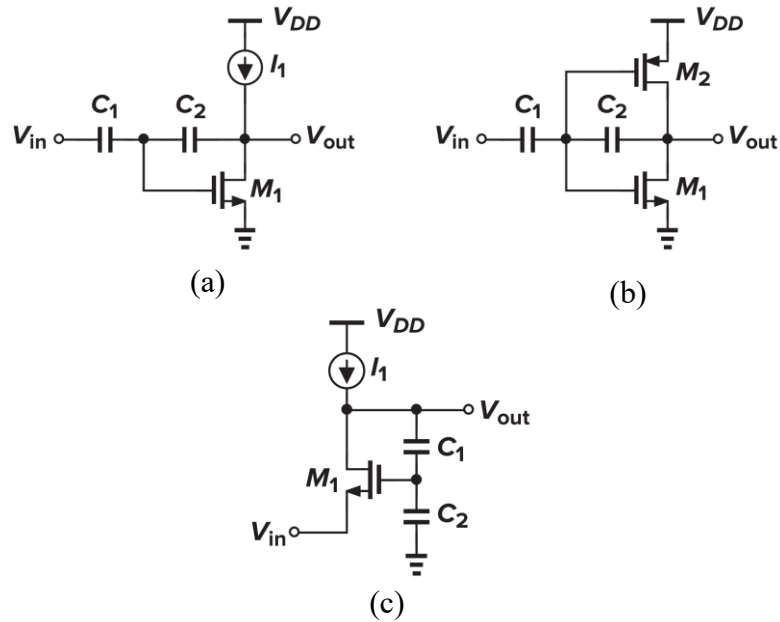


Fig. 1

6.2 In the circuit of Fig. 2, $(W/L)_{1-3} = 50/0.5$, $I_{D1} = |I_{D2}| = |I_{D3}| = 0.5$ mA, and $R_{S1} = R_F = R_{D2} = 2$ k Ω . Neglecting channel length modulation of M_1 and if $\gamma = 0$.

- Determine the input bias voltage required to establish the above currents.**
- Calculate the closed-loop voltage gain and output resistance.**

 


Fig. 2

6.3 In the circuit of Fig. 3, assume that $\lambda = 0$, $g_{m1,2} = 10 \text{ mS}$, $R_{1-3} = 3 \text{ k}\Omega$, and $C_1 = 100 \text{ pF}$. Neglecting channel length modulation and other capacitances, estimate the closed-loop voltage gain at very low and very high frequencies.

 


Fig. 3