

Homework #2 of 「類比積體電路導論」

作業繳交截止日期: Oct. 17, 2024 12:00 (上傳 E3 數位平台繳交)

本次作業共三大題, 2.1~2.3

請將作業轉成一個 PDF 檔案(file size 小於 10MB), 檔名請使用

「AIC_HW2_自己的學號」(例如: AIC_HW2_109700018), 於作業繳

交截止日期/時間前, 上傳到指定的 E3 數位平台繳交。

Unless otherwise stated, in the following problems, use the device data shown in Table 1 and assume that $V_{DD} = 3V$. The Dielectric constant of gate oxide is 3.9 and $\epsilon_o = 8.854 \times 10^{-12} F/m$.

Table 1. Level 1 SPICE models for NMOS and PMOS devices.

NMOS Model			
LEVEL = 1	VTO = 0.7	GAMMA = 0.45	PHI = 0.9
NSUB = 9e+14	LD = 0.08e-6	UO = 350	LAMBDA = 0.1
TOX = 9e-9	PB = 0.9	CJ = 0.56e-3	CJSW = 0.35e-11
MJ = 0.45	MJSW = 0.2	CGDO = 0.4e-9	JS = 1.0e-8
PMOS Model			
LEVEL = 1	VTO = -0.8	GAMMA = 0.4	PHI = 0.8
NSUB = 5e+14	LD = 0.09e-6	UO = 100	LAMBDA = 0.2
TOX = 9e-9	PB = 0.9	CJ = 0.94e-3	CJSW = 0.32e-11
MJ = 0.5	MJSW = 0.3	CGDO = 0.3e-9	JS = 0.5e-8

VTO: threshold voltage with zero V_{SB} (unit: V)

GAMMA: body-effect coefficient (unit: $V^{1/2}$)

PHI: $2\Phi_F$ (unit: V)

TOX: gate-oxide thickness (unit: m)

NSUB: substrate doping (unit: cm^{-3})

LD: source/drain side diffusion (unit: m)

UO: channel mobility (unit: $cm^2/V/s$)

LAMBDA: channel-length modulation coefficient (unit: V^{-1})

CJ: source/drain bottom-plate junction capacitance per unit area (unit: F/m^2)

CJSW: source/drain sidewall junction capacitance per unit length (unit: F/m)

PB: source/drain junction built-in potential (unit: V)

MJ: exponent in CJ equation (unitless)

MJSW: exponent in CJSW equation (unitless)

CGDO: gate-drain overlap capacitance per unit width (unit: F/m)

CGSO: gate-source overlap capacitance per unit width (unit: F/m)

JS: source/drain leakage current per unit area (unit: A/m^2)

- 2.1 Assuming all MOSFETs are in saturation, calculate the small signal voltage gain of each circuit in Fig. 1 ($\gamma = 0, \lambda \neq 0$).

本題限定使用 g_{m_x} , r_{o_x} 電晶體參數符號進行推導 (30 pts)

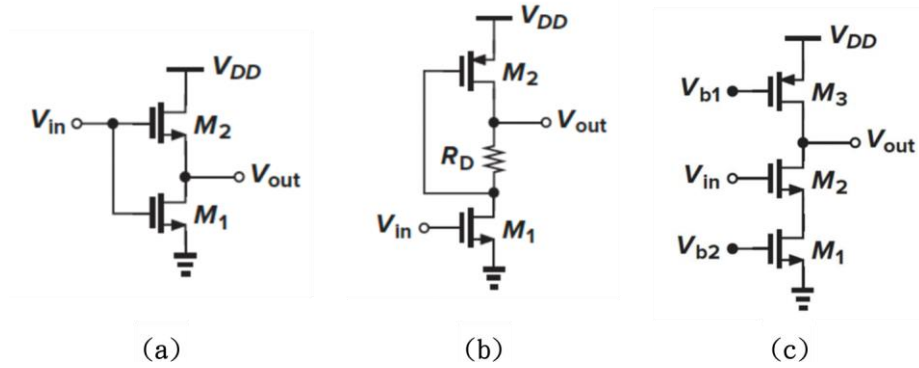


Figure 1

- 2.2 Assuming that all the transistors in the circuits of Fig. 2 are saturated and designed with $(W/L)_{1,2} = 45/0.3$ ($\mu\text{m}/\mu\text{m}$), $(W/L)_{3,4} = 10/0.3$ ($\mu\text{m}/\mu\text{m}$), $R_D = 5$ k Ω , and $(W/L)_5 = 75/1$ ($\mu\text{m}/\mu\text{m}$) with $I_{DS,M5} = 0.5$ mA. Use $\lambda = \gamma = 0$ for bias purpose and $\gamma = 0, \lambda \neq 0$ for small signal analysis. Answer the following questions for each circuit. (45 pts)

- What are the minimum and maximum allowable input common mode voltage levels if the differential swings at the input and output are small?
- What are the maximum allowable output voltage swing if $V_{in,CM} = 1.2$ V?
- What's the differential mode voltage gain if $V_{in,CM} = 1.2$ V?

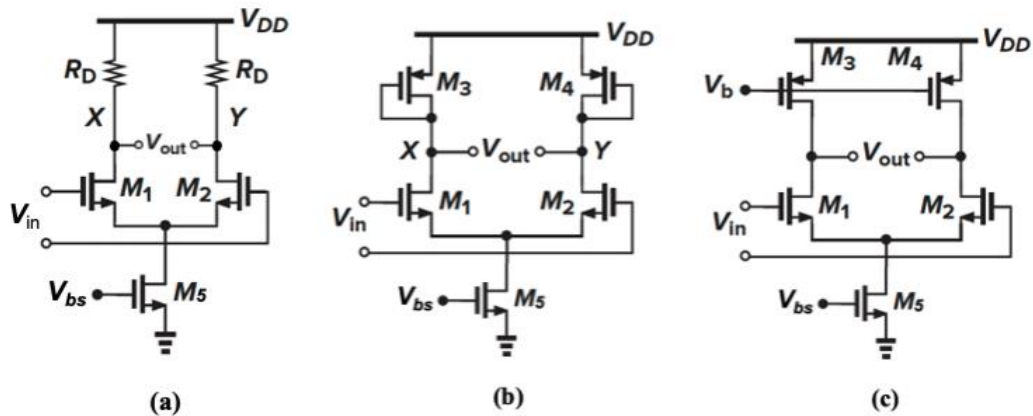


Figure 2

- 2.3 In the circuit of Fig. 3, assume that $I_{SS}=1$ mA, $V_{DD}=3$ V and $W/L=60/0.5$ for all the transistors. Also we have $I_{SD,M5} = I_{SD,M6} = 0.4 \times I_{SS}$. Use $\lambda=\gamma=0$ for bias purpose and $\lambda \neq 0$, $\gamma=0$ for small signal analysis. (25 pts)
- (a) Determine the differential mode voltage gain (V_{out}/V_{in}).
- (b) Calculate V_b such that $I_{SD,M5} = I_{SD,M6} = 0.4 \times I_{SS}$.
- (c) If I_{SS} requires a minimum voltage of 0.4 V, what is the maximum differential output swing?

 


Figure 3